

Quiz 09 IR Transmitter and Receiver

總分 100/100 ?

NCTU EELAB Fall

區段分數 0/0

Class *

☐ DEE222

☒ DEE320

Student ID *

0710175

Name *



陳愉方

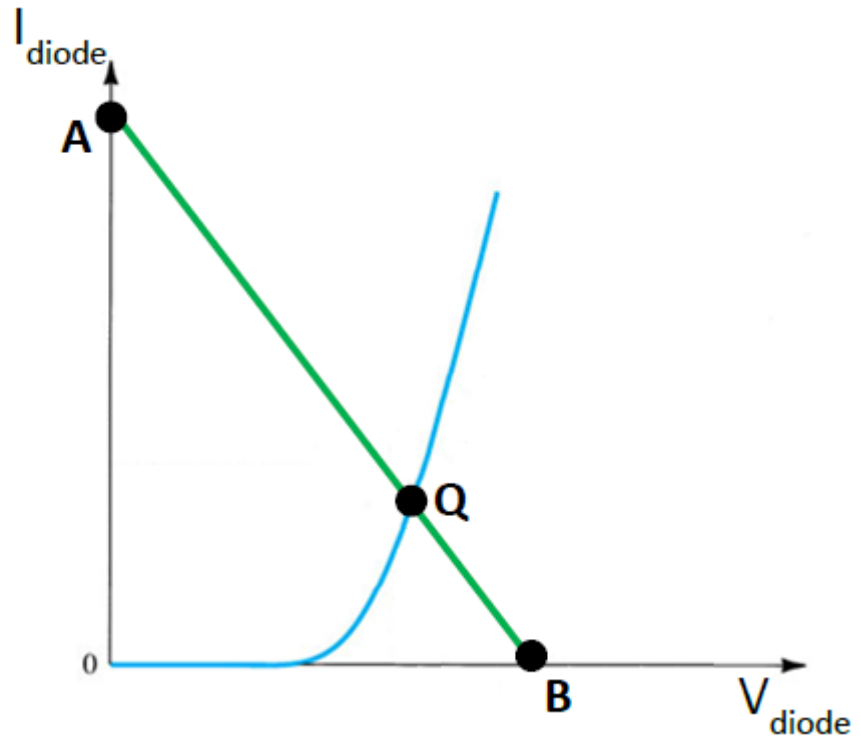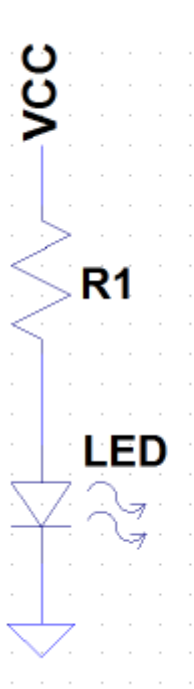Q1. Look at the figures below, answer the following questions about load line.

區段分數 20/20



HINT : Apply KVL, $V_{CC} = I_{diode} \cdot R_1 + V_{diode}$



✓ Idiode = ? *

5/5

$$\frac{1}{R_1} V_{CC}$$

☐ 選項 1

$$R_1 V_{diode} - \frac{1}{R_1} V_{CC}$$

☐ 選項 2

$$-\frac{1}{R_1} V_{diode} + \frac{1}{R_1} V_{CC}$$

☒ 選項 3

$$\frac{1}{R_1} V_{diode} + R_1 V_{CC}$$

☐ 選項 4

✓ point A = ? *

5/5

$$\frac{1}{R_1} V_{CC}$$

☒ 選項 1☐ 選項 2

$$R_1 V_{\text{diode}}$$

$$-R_1 V_{CC}$$

☐ 選項 3

$$-\frac{1}{R_1} V_{\text{diode}}$$

☐ 選項 4

✓ point B = ? *

5/5

$$V_{CC}$$

$$\frac{1}{R_1} V_{CC}$$

☒ 選項 1

☐ 選項 2

$$-\frac{1}{R_1} V_{\text{diode}}$$

$$R_1 V_{\text{diode}}$$

☐ 選項 3

☐ 選項 4

✓ point Q is usually called ? *multi-choice *

5/5

☐ saturation point

☒ bias point

☐ amplification point


☒ operation point


Q2. Look at the figures below, answer the following questions





about operation point.

區段分數 40/40

Circuit

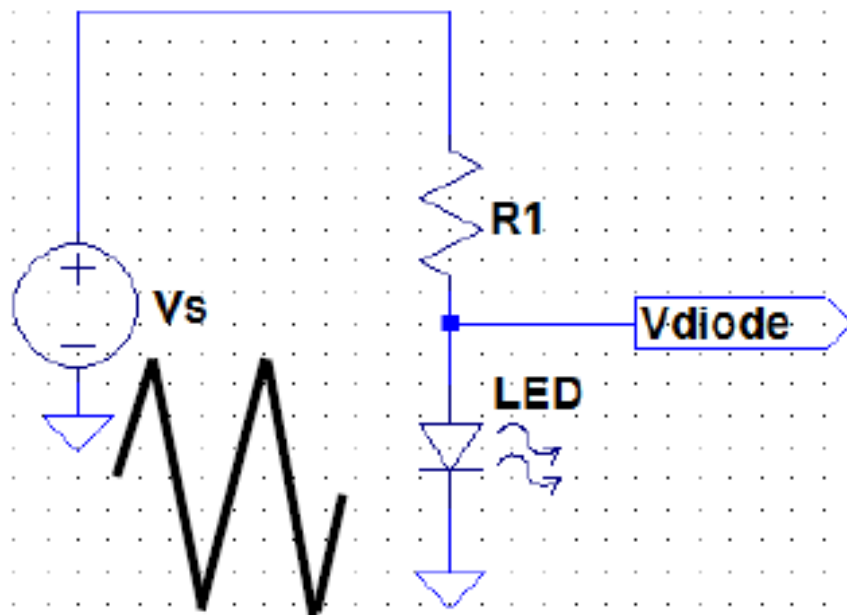

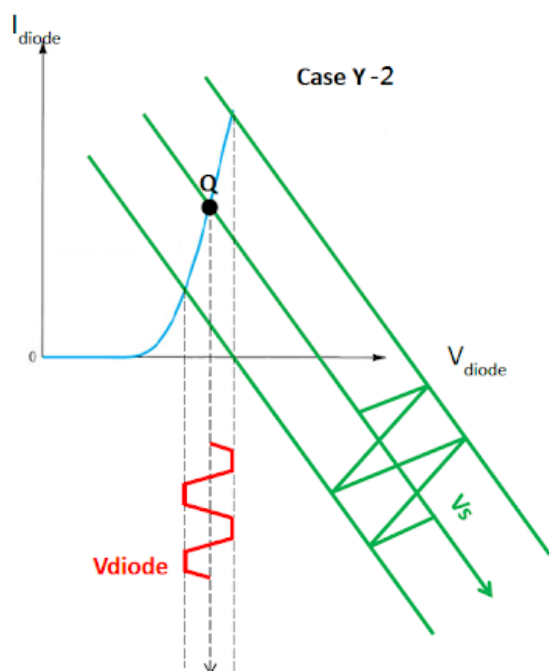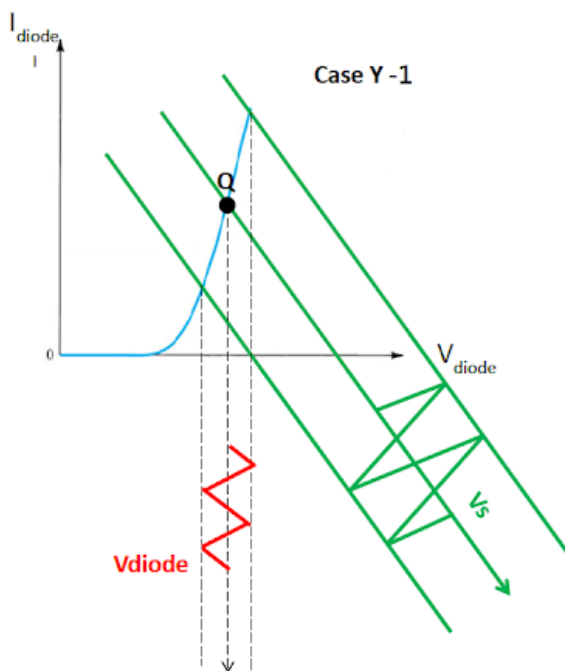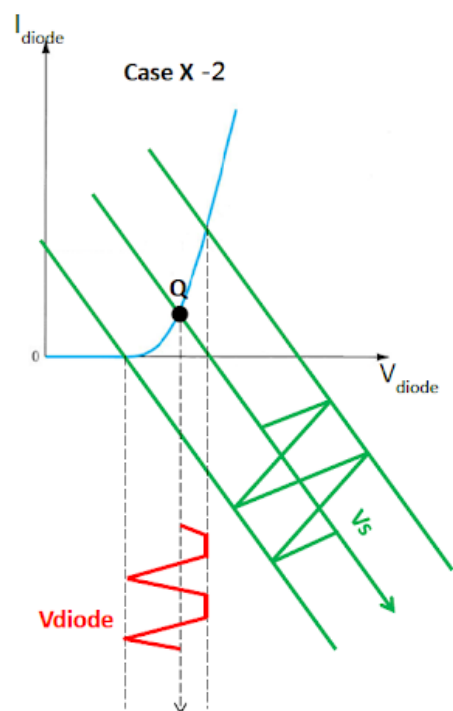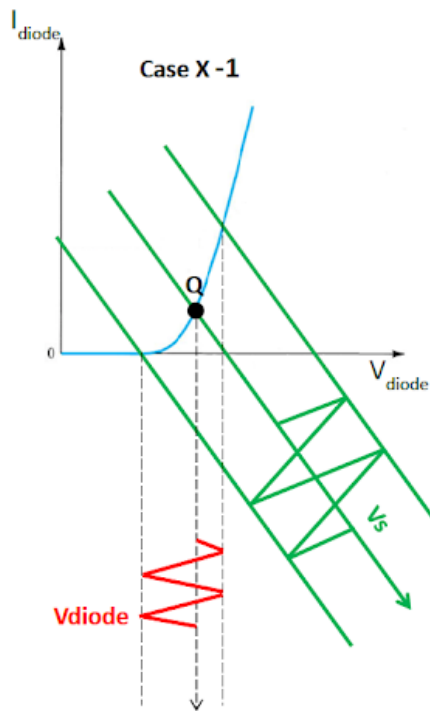✓ Choose the most possible V_{diode} waveform about different cases of operation point. *multi-choice *



☐ Case X -1

☒ Case X -2

☒ Case Y -1

☐ Case Y -2

✓

✓

✓ which case could be considered as a "good operation point?" *

10/10

☐ Case X

☒ Case Y



Q3. NPN BJT 3904.


區段分數 10/10



✓ Match pins of NPN BJT 3904. *

10/10

2N3904 NPN General Purpose Amplifier

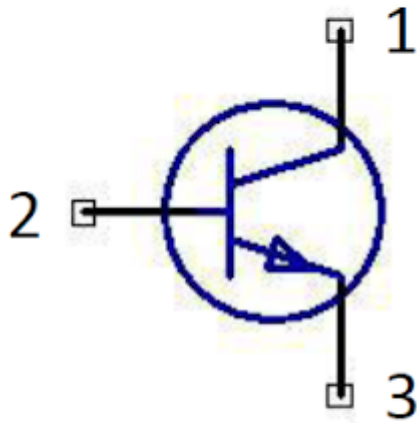

E = EMITTER
C = COLLECTOR
B = BASE




www.electroniccircuits.com

- ☐ (E,B,C) = (1,2,3)
- ☒ (E,B,C) = (3,2,1)
- ☐ (E,B,C) = (2,1,3)
- ☐ (E,B,C) = (3,1,2)
- ☐ (E,B,C) = (1,3,2)

✓

Q4. Look at the CE circuit below, follow the steps and derive R1.

區段分數 30/30

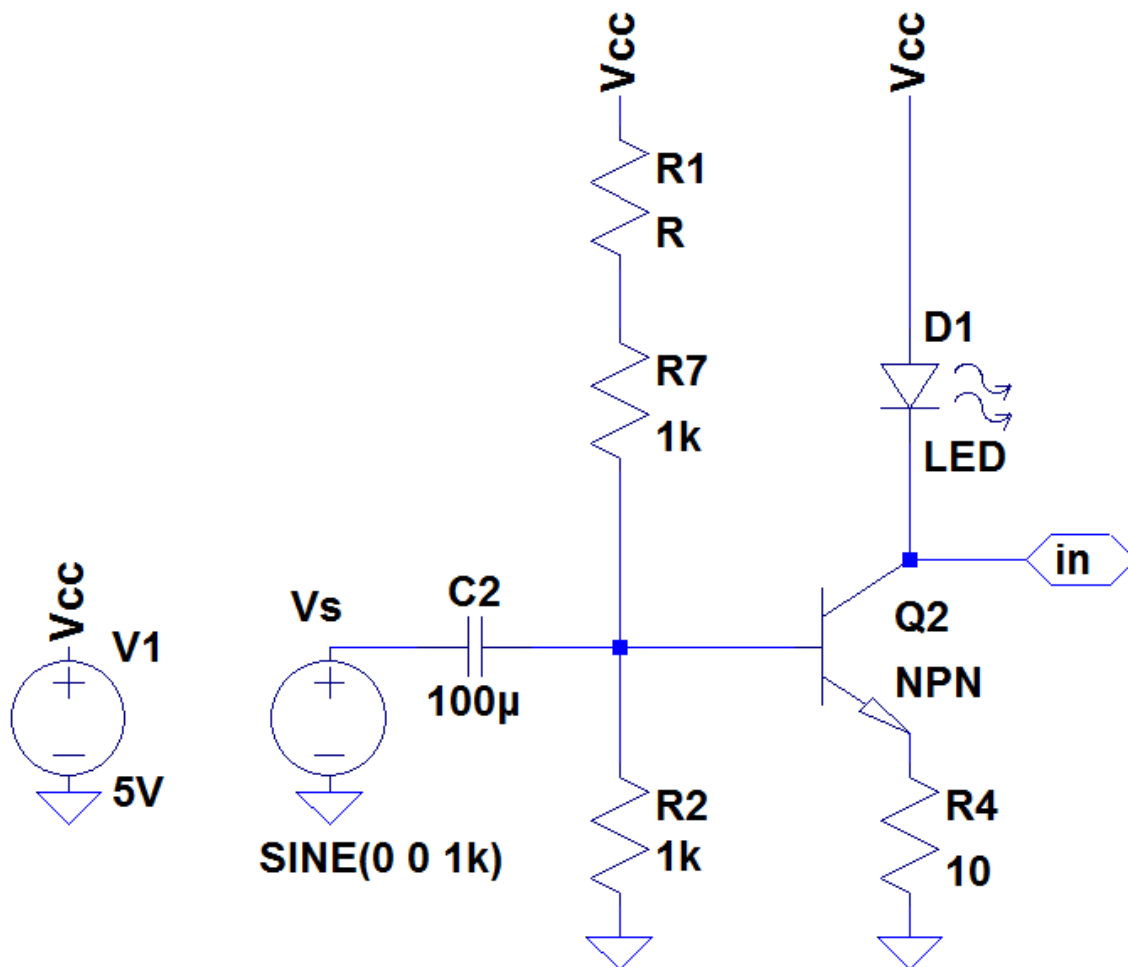Design conditions : $V_E = 0.5V$, $\beta = 200$ ✓ $I_C = ?$ *

5/5

Step1. $I_C \cong I_E = ?$

- ☐ 0.5 A
- ☒ 0.05 A
- ☐ 0.005 A

✓

✓ IB = ? *

5/5

$$\text{Step2. } I_B = \frac{I_C}{\beta} = ?$$

- ☐ 2.5 mA
- ☐ 0.025 A
- ☒ 0.25 mA

✓

✓ VB = ? *

5/5

$$\text{Step3. } V_B = V_E + 0.7V = ?$$

- ☐ 0.7 V
- ☐ 0.5 V
- ☒ 1.2 V

✓

✓ IR2 = ? *

5/5

$$\text{Step4. } I_{R2} = \frac{V_B}{R_2} = ?$$

- ☐ 0.7 A
- ☐ 0.05 A
- ☒ 1.2 mA

✓



✓ IR1 = ? *

5/5

$$\text{Step5. } I_{R1} = I_B + I_{R2} = ?$$

- ☐ 0.75 A
- ☒ 1.45 mA
- ☐ 0.25 A

✓

✓ R1 = ? *

5/5

$$\text{Step6. } R_1 = \frac{V_{CC} - V_B}{I_{R1}} - R_7 = ?$$

- ☐ 300 Ω
- ☒ 1600 Ω
- ☐ 5000 Ω

✓

這份表單是在 國立交通大學 中建立。

Google 表單

