
REPORT

 Experiment 1: Photointerrupter characteristic



How does a photointerrupter work?


A photointerrupter consists of two main components: a light source (typically an LED) and a light detector (usually a phototransistor or photodiode). These two components are arranged in a way that the light from the source can reach the detector. When an object causes changes in the amount of light reaching the detector, there's a corresponding change in the output signal.


Observation:


The transistor on the photointerruptor acts as a lowpass filter, allowing frequencies below 450 Hz to pass through unattenuated.

Experiment 2: Active band pass filter

	Specified N	Vode DC value	
U1,V+ (V)	U1,Vout (V)	U2,V+(V)	U2,Vout (V)
1.65	1.65	1.66	1.66
	AC SWEE	EP Waveform	
MSO5074 Tue March 19 20	0:30:58 2024		
RIGOL STOP	H 2.00s 1MSa/s Measu	re STOP/RUN D 0.00s	T ♣ 1 1.76V A
			
Ē			
		4	
	\ \ \ \ \ \ \ \ \ \ \ \ \ \ \ \ \ \ \	\ <u>\</u>	/ / / / / / / / / / / / / / / / / / /
T	V V '		\bigvee
2			
		游	標 (*)
E		AX:	
-		AY:	-1.9s
E		BY: ΔX:	4.06s
平均值2 頻率2	頻率1	ΔY:	850mV xX: 246.3mHz
平均恒2 頻率2 1.6611V 100.27r			
1 == 2.00V 0.00V	2 == 1.00V 0.00V 3 == 100mV 0.00V	100mV 0.00V 0 1 2 3 4 5 6 7 8 9 1011 12131415	GI GII

 

 

 

Observation:

According to my LTspice simulation, this bandpass filter has a **lower cutoff frequency** of approximately **0.35Hz** and an **upper cutoff frequency** of approximately **3.71Hz**. It's **passband gain** is around **33dB**, which will allow us to greatly amplify the signal coming from the photointerrupter.

Experiment 3: Heart Rate Monitor



Observation:

The Channel 1 (Yellow) signal is the original unamplified signal from the photointerrupter. It's extremely small in amplitude, therefore it's swings are barely visible on screen. The Channel 2 (Blue) signal is the result of the photointerrupter's signal passed through the bandpass filter from exp2. **Undesired** frequencies are attenuated and the frequency containing the information of my heart rate is amplified by approximately 33dB.

Experiment 4: Parking Radar

Video link

https://www.youtube.com/shorts/xK1ARda4v2s

(optional) Attach your code here.

```
int trigPin = 11;
int echoPin = 12;
int speakerpin = 6;
long duration, cm;
void setup() {
  Serial.begin (9600);
  pinMode(trigPin, OUTPUT);
  pinMode(echoPin, INPUT);
  pinMode(speakerpin, OUTPUT);
void loop()
  digitalWrite(trigPin, LOW);
  delayMicroseconds(5);
  digitalWrite(trigPin, HIGH);
  delayMicroseconds(10);
  digitalWrite(trigPin, LOW);
  pinMode(echoPin, INPUT);
  duration = pulseIn(echoPin, HIGH);
  cm = (duration/2) / 29.1;
  Serial.print(cm);
  Serial.println(" cm");
  if (cm <= 5) {
    analogWrite(speakerpin, 200);
    delay (25);
    digitalWrite(speakerpin, 0);
    delay (25);
  if (cm > 5 && cm <= 10) {
    analogWrite(speakerpin, 200);
```

```
delay (50);
  digitalWrite(speakerpin, 0);
  delay (50);
 if (cm > 10 && cm <= 15) {
  analogWrite(speakerpin, 200);
  delay (100);
  digitalWrite(speakerpin, 0);
  delay (100);
if (cm > 15 && cm <= 20) {
  analogWrite(speakerpin, 200);
  delay (250);
  digitalWrite(speakerpin, 0);
  delay (250);
if (cm > 15 && cm <= 20) {
  digitalWrite(speakerpin, 0);
  delay (100);
```

Code Explanation:

The code used here is fairly intuitive. I utilized the **analogWrite() function to generate a PWM signal of around 490 Hz** and pass it to the speaker. The delay() function is used to control the interval between beeps. Smaller time intervals are used as the distance between the HC-SR04 and the approaching object gets smaller.

How does the function "analogWrite()" work?

The "analogWrite()" function takes 2 parameters, the 1st is the output pin. Only ports with '~' are capable of PWM, so only ports ~3, ~5, ~6, ~9, ~10, ~11 on the Uno board are compatible with this function. The 2nd parameter dictates the duty cycle of the PWM signal. There is an internal counter that counts from 0 to 255, then resets to 0 and starts counting again. The number parameter provided tells Arduino to set the output as "HIGH" before counting to the given number.

Examples:

- i. analogWrite(3, 127); means that pin3 will output HIGH while the number of the counter is 0~127; it will output LOW during 127~255. This produces a 50% duty cycle signal.
- ii. analogWrite(3, 64); means that pin3 will output HIGH while the number of the counter is 0~64; it will output LOW during 64~255. This produces a 25% duty cycle signal.
- iii. analogWrite(3, 0); means that pin3 will always be LOW.
- iv. analogWrite(3, 255); means that pin3 will always be HIGH.

To get the desired duty cycle you simply multiply the duty cycle you desire by 255 and pass the result in as parameter. Ex: Desired Duty Cycle: 75% analogWrite() $Param = 255 \times 75\% = 191.25 \approx 191$

Reference:

- 1. ROHM Semiconductor: https://www.rohm.com/products/faq-search/faqId/279
- 2. ElectronicsTutorials: https://www.electronics-tutorials.ws/filter/filter_7.html
- 3. Ray 的 Arduino 教學:

https://sites.google.com/view/rayarduino/%E8%B6%85%E9%9F%B3%E6%B3%A2%E8%B7%9D%E9%9B%A2%E6%84%9F%E6%B8%AC%E5%99%A8