

## ***Chapter 12: Bandgap References***


- 12.1 General Considerations**
- 12.2 Supply-Independent Biasing**
- 12.3 Temperature-Independent References**
- 12.4 PTAT Current Generation**
- 12.5 Constant- $G_m$  Biasing**
- 12.6 Speed and Noise Issues**
- 12.7 Low-Voltage Bandgap References**
- 12.8 Case Study**

# General Considerations

- Objective of reference generation is to establish a dc voltage or current independent of the supply and process and has a well-defined behavior with temperature
- Three forms of temperature dependence:
  - Proportional to absolute temperature (PTAT)
  - Constant- $G_m$  behavior, i.e., such that the transconductance of certain transistors remains constant
  - Temperature independent
- Two design problems:
  - Supply-independent biasing
  - Definition of temperature variation
 
# Supply-Independent Biasing

- Use of bias currents and current mirrors implicitly assumes a “golden” reference current is available
- As shown in Fig. (a), if  $I_{REF}$  does not vary with  $V_{DD}$ , and channel-length modulation of  $M_2$  and  $M_3$  is neglected, then  $I_{D2}$  and  $I_{D3}$  remain independent of the supply voltage
- How to generate  $I_{REF}$ ?




## Supply-Independent Biasing

- As an approximation of a current source, we tie a resistor from  $V_{DD}$  to the gate of  $M_1$  [Fig. (b)]
- Output current of this circuit is quite sensitive to  $V_{DD}$ :

$$\Delta I_{out} = \frac{\Delta V_{DD}}{R_1 + 1/g_{m1}} \cdot \frac{(W/L)_2}{(W/L)_1}$$

 
- To arrive at a less sensitive solution, we postulate that the circuit must bias itself, i.e.,  $I_{REF}$  must somehow be derived from  $I_{out}$



(b)

 
# Supply-Independent Biasing

- If  $I_{out}$  is to be independent of  $V_{DD}$ , then  $I_{REF}$  can be a replica of  $I_{out}$
- In circuit below,  $M_3$  and  $M_4$  copy  $I_{out}$ , thus defining  $I_{REF}$
- $I_{REF}$  is “bootstrapped” to  $I_{out}$
- Here,  $I_{out} = K I_{REF}$  if channel-length modulation is neglected
- Since each diode-connected device feeds from a current source,  $I_{out}$  and  $I_{REF}$  are relatively independent of  $V_{DD}$



 
# Supply-Independent Biasing

- If  $M1 - M4$  operate in saturation and  $\lambda \approx 0$ , the circuit is governed by only one equation,  $I_{out} = K I_{REF}$ , and hence can support any current level
- If we initially force  $I_{REF}$  to be  $10 \mu A$ , the resulting  $I_{out}$  of  $K \times 10 \mu A$  “circulates” around the loop, sustaining these current levels in the left and right branches indefinitely



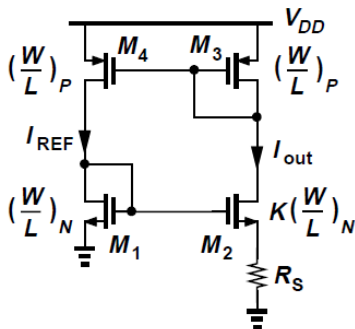
# Supply-Independent Biasing

- To uniquely define the currents, we add another constraint to the circuit as in Fig. (a)
- Resistor  $R_S$  decreases the current of  $M_2$  while the PMOS devices need  $I_{out} = I_{REF}$  due to identical dimensions and thresholds



(a)

# Supply-Independent Biasing

 

(a)

- We can write,  $V_{GS1} = V_{GS2} + I_{D2}R_S$ ,  
or,

$$\sqrt{\frac{2I_{out}}{\mu_n C_{ox}(W/L)_N}} + V_{TH1} = \sqrt{\frac{2I_{out}}{\mu_n C_{ox}K(W/L)_N}} + V_{TH2} + I_{out}R_S$$

- Neglecting body effect,

$$\sqrt{\frac{2I_{out}}{\mu_n C_{ox}(W/L)_N}} \left(1 - \frac{1}{\sqrt{K}}\right) = I_{out}R_S$$

- Hence,


$$I_{out} = \frac{2}{\mu_n C_{ox}(W/L)_N} \cdot \frac{1}{R_S^2} \left(1 - \frac{1}{\sqrt{K}}\right)^2$$

- As expected, the current is independent of the supply voltage (but still a function of process and temperature)


 
# Supply-Independent Biasing


- The assumption  $V_{TH1} = V_{TH2}$  introduces some error in the foregoing calculations because sources of  $M1$  and  $M2$  are at different voltages
- Simple remedy is to place the resistor at the source of  $M3$  while eliminating body effect by tying the source and bulk of each PMOS
- Relatively long channel lengths are used for all transistors in the circuit



(b)
 
# Supply-Independent Biasing


- Important issue in supply-independent biasing is the existence of “degenerate” bias points
- In circuit of Fig. (a), if all transistors carry zero current when supply is turned on, they remain off indefinitely
- Loop can support zero current in both branches
- Circuit can settle in one of two different operating conditions
- Called the “start-up” problem



(a)


# Supply-Independent Biasing

- Start-up problem can be solved by adding a mechanism to drive the circuit out of degenerate bias point when supply is turned on
- In Fig. (a), diode-connected device  $M_5$  provides a current path from  $V_{DD}$  through  $M_3$  and  $M_1$  to ground upon start-up
- $M_3$  and  $M_1$ , and hence  $M_2$  and  $M_4$ , cannot remain off
- This technique is practical only if  $V_{TH1} + V_{TH5} + |V_{TH3}| < V_{DD}$  and  $V_{GS1} + V_{TH5} + |V_{GS3}| > V_{DD}$  to ensure  $M_5$  remains off after start-up

 

# Supply-Independent Biasing

 - Problem of start-up requires careful analysis and simulation
- Supply voltage must be ramped from zero in a dc sweep simulation (such that parasitic capacitances do not cause false start-up) as well as in a transient simulation
- Behavior of the circuit must be examined for each supply voltage



(b)

# Temperature-Independent References

- Reference voltages or currents exhibiting little dependence of temperature are useful in analog circuits
- If two quantities having opposite temperature coefficients (TCs) are added with proper weighting, the result displays a zero TC
- For two voltages  $V_1$  and  $V_2$  that vary in opposite directions with temperature, we choose  $\alpha_1$  and  $\alpha_2$  such that  $\alpha_1 \partial V_1 / \partial T + \alpha_2 \partial V_2 / \partial T = 0$ , obtaining a reference voltage,  $V_{REF} = \alpha_1 V_1 + \alpha_2 V_2$ , with zero TC
- Characteristics of bipolar transistors have proven the most reproducible and well-defined quantities that can provide positive and negative TCs

## Negative-TC Voltage

- The base-emitter voltage of bipolar transistors, or more generally, the forward voltage of a *pn*-junction diode exhibits a negative TC
- For a bipolar device,  $I_C = I_S \exp(V_{BE}/V_T)$ , where  $V_T = kT/q$
- Saturation current  $I_S$  is proportional to  $\mu k T n_i^2$ , where  $\mu$  denotes the mobility of minority carriers and  $n_i$  is the intrinsic carrier concentration of silicon
- The temperature dependence of these quantities is expressed as  $\propto T^m$ , where  $m \approx -3/2$ , and  $n_i^2 \propto T^3 \exp[-E_g/(kT)]$ , where  $E_g \approx 1.12$  eV is the bandgap energy of silicon
- Thus,

$$I_S = b T^{4+m} \exp \frac{-E_g}{kT}$$

where  $b$  is proportional to  $\mu n_i^2$

# Negative-TC Voltage

- Writing  $V_{BE} = V_T \ln(I_C/I_S)$ , we can now compute the TC of the base-emitter voltage
- For simplicity, we assume  $I_C$  is held constant
- Thus,

$$\frac{\partial V_{BE}}{\partial T} = \frac{\partial V_T}{\partial T} \ln \frac{I_C}{I_S} - \frac{V_T}{I_S} \frac{\partial I_S}{\partial T}$$

- Using expression derived for  $I_S$ ,

$$\frac{\partial I_S}{\partial T} = b(4+m)T^{3+m} \exp \frac{-E_g}{kT} + bT^{4+m} \left( \exp \frac{-E_g}{kT} \right) \left( \frac{E_g}{kT^2} \right)$$

- Therefore,

- Thus,

$$\frac{V_T}{I_S} \frac{\partial I_S}{\partial T} = (4+m) \frac{V_T}{T} + \frac{E_g}{kT^2} V_T$$

$$\begin{aligned} \frac{\partial V_{BE}}{\partial T} &= \frac{V_T}{T} \ln \frac{I_C}{I_S} - (4+m) \frac{V_T}{T} - \frac{E_g}{kT^2} V_T \\ &= \frac{V_{BE} - (4+m)V_T - E_g/q}{T} \end{aligned}$$

## Negative-TC Voltage


- TC of the base-emitter voltage at a given temperature  $T$  depends on the magnitude of  $V_{BE}$  itself
- With  $V_{BE} \approx 750$  mV and  $T = 300$  K, we have  

$$\partial V_{BE} / \partial T \approx -1.5 \text{ mV/K}$$
- In old bipolar technologies, where  $I_C/I_S$  was relatively small,  $V_{BE} \approx 700$  mV and  $\partial V_{BE} / \partial T \approx -1.9 \text{ mV/K}$  at room temperature
- Modern bipolar transistors operate at much higher current densities, exhibiting  $V_{BE} \approx 800$  mV and hence  

$$\partial V_{BE} / \partial T \approx -1.5 \text{ mV/K} \quad \text{at } T = 300 \text{ K}$$
- TC of  $V_{BE}$  itself depends on temperature, creating error in constant reference generation if the positive-TC quantity exhibits a constant (positive) TC



# Positive-TC Voltage

 

If two BJTs operate at unequal current densities, the difference between their base-emitter voltages is directly proportional to the absolute temperature

- As shown, if two identical transistors ( $I_{S1} = I_{S2}$ ) are biased at collector currents of  $nI_0$  and  $I_0$  and their base currents are negligible,

$$\begin{aligned}\Delta V_{BE} &= V_{BE1} - V_{BE2} \\ &= V_T \ln \frac{nI_0}{I_{S1}} - V_T \ln \frac{I_0}{I_{S2}} \\ &= V_T \ln n.\end{aligned}$$

- Thus,  $V_{BE}$  difference exhibits a positive-TC

$$\frac{\partial \Delta V_{BE}}{\partial T} = \frac{k}{q} \ln n$$

## Bandgap Reference


- With positive and negative-TC voltages, we can develop a reference having a nominally zero TC
- We write  $V_{REF} = \alpha_1 V_{BE} + \alpha_2 (V_T \ln n)$ , where  $V_T \ln n$  is the difference between the base-emitter voltages of two BJTs operating at different current densities
- At room temperature,  $\partial V_{BE} / \partial T \approx -1.5 \text{ mV/K}$  whereas  $\partial V_T / \partial T \approx +0.087 \text{ mV/K}$ , we set  $\alpha_1 = 1$  and choose  $\alpha_2 \ln n$  such that  $(\alpha_2 \ln n)(0.087 \text{ mV/K}) = 1.5 \text{ mV/K}$
- That is,  $\alpha_2 \ln n \approx 17.2$ , indicating that, for a zero TC:

$$\begin{aligned} V_{REF} &\approx V_{BE} + 17.2 V_T \\ &\approx 1.25 \text{ V.} \end{aligned}$$

- Need to devise a circuit that adds  $V_{BE}$  to  $17.2 V_T$
 
# Bandgap Reference


- Consider the circuit shown below
- Base currents are assumed negligible
- Transistor  $Q_2$  consists of  $n$  unit transistors in parallel, and  $Q_1$  is a unit transistor
- If somehow  $V_{O1}$  and  $V_{O2}$  are forced to be equal, then  $V_{BE1} = RI + V_{BE2}$  and  $RI = V_{BE1} - V_{BE2} = VT \ln n$
- Thus,  $V_{O2} = V_{BE2} + VT \ln n$ , suggesting that  $V_{O2}$  can serve as a temperature-independent reference if  $\ln n \approx 17.2$  (while  $V_{O1}$  and  $V_{O2}$  remain equal)



## Bandgap Reference


- Three modifications needed for previous circuit to be practical:
  - 1) A mechanism must be added to guarantee  $V_{O1} = V_{O2}$
  - 2) Since  $\ln n = 17.2$  translates to a prohibitively large  $n$ , the term  $RI = VT \ln n$  must be scaled up by a reasonable factor
  - 3)  $V_{O2}$  cannot become temperature-independent because  $V_{O2} \approx V_{BE1} \approx 800 \text{ mV}$  whereas for temperature-independence,  
 $V_{O2} = V_{BE2} + 17.2VT \approx 1.25 \text{ V}$

# Bandgap Reference

 

- Above implementation accomplishes all three tasks
- Amplifier  $A_1$  senses  $V_X$  and  $V_Y$ , driving the top terminals of  $R_1$  and  $R_2$  ( $R_1 = R_2$ ) such that  $X$  and  $Y$  settle to approximately equal voltages
- The reference voltage is obtained at output of the amplifier (rather than at node  $Y$ )

# Bandgap Reference

 


- Following earlier analysis,  $V_{BE1} - V_{BE2} = V_T \ln n$ , arriving at a current of  $V_T \ln n / R_3$  through the right branch and hence an output voltage of

$$\begin{aligned} V_{out} &= V_{BE2} + \frac{V_T \ln n}{R_3} (R_3 + R_2) \\ &= V_{BE2} + (V_T \ln n) \left( 1 + \frac{R_2}{R_3} \right) \end{aligned}$$

- For a zero  $\alpha$ , we must have  $(1 + R_2/R_3) \ln n \approx 17.2$ , for example  $n = 31$  and  $R_2/R_3 = 4$

# Bandgap Reference: Issues

 

## (1) Collector Current Variation:

• Circuit violates earlier assumption:  $I_{C1}$  and  $I_{C2}$ , given by  $(V_T \ln n)/R_3$ , are proportional to  $T$ , whereas

$$\frac{\partial V_{BE}}{\partial T} \approx -1.5 \text{ mV/K}$$

constant current

• Assume  $I_{C1} = I_{C2} \square (V_T \ln n)/R_3$

- Including  $\partial I_C / \partial T$  in the equation for TC of  $V_{BE}$ ,

$$\frac{\partial V_{BE}}{\partial T} = \frac{\partial V_T}{\partial T} \ln \frac{I_C}{I_S} + V_T \left( \frac{1}{I_C} \frac{\partial I_C}{\partial T} - \frac{1}{I_S} \frac{\partial I_S}{\partial T} \right)$$

- Since  $\partial I_C / \partial T \approx (V_T \ln n) / (R_3 T) = I_C / T$ ,

$$\frac{\partial V_{BE}}{\partial T} = \frac{\partial V_T}{\partial T} \ln \frac{I_C}{I_S} + \frac{V_T}{T} - \frac{V_T}{I_S} \frac{\partial I_S}{\partial T}$$


- Thus, the TC is slightly less negative than -1.5 mV/K

$$\frac{\partial V_{BE}}{\partial T} = \frac{V_{BE} - (3 + m)V_T - E_g/q}{T}$$

# Bandgap Reference: Issues
 
## (2) Compatibility with CMOS Technology:

- We must seek structures in a standard CMOS technology that exhibit negative- and positive-TC characteristics
- In  $n$ -well processes, a  $pnp$  transistor can be formed as depicted below
- A  $p^+$  region (same as S/D region of PFETs) inside an  $n$ -well serves as the emitter and the  $n$ -well itself as the base
- The  $p$ -type substrate acts as the collector and is connected to the most negative supply (usually ground)






# Bandgap Reference: Issues
 
## (2) Compatibility with CMOS Technology:

- The circuit can be redrawn as shown below




## Bandgap Reference: Issues
 
### (3) Op-Amp Offset and Output Impedance:

- Op amps suffer from input “offsets”, i.e., the output voltage of the op amp is not zero if the input is zero
- Input offset voltage introduces error in the output voltage
- Included below, the effect is quantified as

$$V_{BE1} - V_{OS} \approx V_{BE2} + R_3 I_{C2}$$



# Bandgap Reference: Issues


## (3) Op-Amp Offset and Output Impedance:

•Thus,

$$\begin{aligned}V_{out} &= V_{BE2} + (R_3 + R_2) \frac{V_{BE1} - V_{BE2} - V_{OS}}{R_3} \\&= V_{BE2} + \left(1 + \frac{R_2}{R_3}\right) (V_T \ln n - V_{OS}),\end{aligned}$$

•It is assumed that  $IC2 \square IC1$  despite the offset voltage

 • $V_{OS}$  is amplified by  $1+R_2/R_3$ , introducing error in  $V_{out}$



## Bandgap Reference: Issues


### (3) Op-Amp Offset and Output Impedance:

- Several methods employed to lower the effect of  $V_{OS}$
- First, op amp incorporates large devices in a carefully chosen topology to lower the offset
- Second, the collector currents of  $Q1$  and  $Q2$  can be ratioed by a factor of  $m$  such that  $\Delta V_{BE} = V_T \ln(mn)$
- Third, each branch may use two  $pn$  junctions in series to double  $\Delta V_{BE}$

# Bandgap Reference: Issues
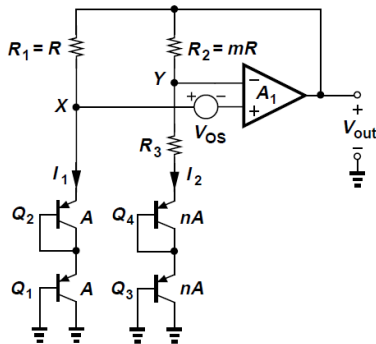
## (3) Op-Amp Offset and Output Impedance:

- Circuit below shows a realization using last two techniques
- $R_1$  and  $R_2$  are ratioed by a factor of  $m$ , so  $I_1 = mI_2$
- Neglecting base currents and assuming  $A_1$  is large, we can write  $V_{BE1} + V_{BE2} - V_{OS} = V_{BE3} + V_{BE4} + R_3I_2$  and  $V_{out} = V_{BE3} + V_{BE4} + (R_3+R_2)I_2$



### **(3) Op-Amp Offset and Output Impedance:**

**•It follows that**


$$\begin{aligned}V_{out} &= V_{BE3} + V_{BE4} + (R_3 + R_2) \frac{2V_T \ln(mn) - V_{OS}}{R_3} \\&= 2V_{BE} + \left(1 + \frac{R_2}{R_3}\right) [2V_T \ln(mn) - V_{OS}].\end{aligned}$$

- The effect of  $V_{OS}$  is reduced by the first term in brackets**
- However,  $V_{out} \approx 2 \approx 1.25 \text{ V} = 2.5 \text{ V}$ , a value difficult to generate by the op amp at low supply voltages**
- In these circuit, the op amp drives two resistive branches and hence, must provide a low output impedance**

# Bandgap Reference: Issues
 
## (3) Op-Amp Offset and Output Impedance:


- The implementation shown on slide 29 is not feasible since collectors of  $Q_2$  and  $Q_4$  are not grounded
- To use the bipolar structure of CMOS, we modify the series combination of the diodes shown in Fig. (a), converting one of the diodes to an emitter follower
- Both transistors are biased by a PMOS current source rather than a resistor to ensure uniform behavior with temperature [Fig. (b)]



# Bandgap Reference: Issues
 
## (3) Op-Amp Offset and Output Impedance:

- Overall circuit is shown below, where the op amp adjusts the gate voltage of the PMOS devices so as to equalize  $V_X$  and  $V_Y$
- Op amp does not experience resistive loading, but the mismatch and channel-length modulation of the PMOS devices introduce error at the output
- Low current gain of the “native” *pnp* transistors





# Bandgap Reference: Issues

## (4) Feedback Polarity:


• In circuit below, feedback signal produced by the op amp returns to both of its inputs, negative feedback factor is given by

$$\beta_N = \frac{1/g_{m2} + R_3}{1/g_{m2} + R_3 + R_2}$$

• **Positive feedback factor is**

$$\beta_P = \frac{1/g_{m1}}{1/g_{m1} + R_1}$$

 • To ensure an overall negative feedback,  $\beta_P$  must be less than  $\beta_N$ , roughly by a factor of two



# Bandgap Reference: Issues

## (5) Bandgap Reference:

- To understand the origin of the terminology “bandgap reference”, we rewrite the output voltage equation

$$V_{REF} = V_{BE} + V_T \ln n$$

- Hence

$$\frac{\partial V_{REF}}{\partial T} = \frac{\partial V_{BE}}{\partial T} + \frac{V_T}{T} \ln n$$

- Setting this to zero and substituting for  $\frac{\partial V_{BE}}{\partial T}$

- Substituting for  $\frac{V_{BE} - (4 + m)V_T - E_g/q}{T} = -\frac{V_T}{T} \ln n$  in the equation,


- $V_{REF}$  is given by  $V_{REF} = \frac{E_g}{q} + (4 + m)V_T$  numbers: the bandgap voltage of silicon,  $E_g/q$ , the temperature exponent of mobility,  $m$ , and the thermal voltage  $V_T$

- The term “bandgap” is used because as  $T \rightarrow 0$ ,  $V_{REF} \rightarrow E_g/q$

# Bandgap Reference: Issues
 
## (6) Supply Dependence and Start-Up:



- In the circuit below, output voltage is relatively independent of supply voltage as long as open-loop gain of the op amp is sufficiently high
- Circuit may require a start-up mechanism because if  $V_X$  and  $V_Y$  are equal to zero, the input differential pair of the op amp may turn off
- Supply rejection of the circuit typically degrades at high frequencies, mandating “supply regulation”





# Bandgap Reference: Issues
  
## (7) Curvature Correction:

- Bandgap voltages exhibit a finite “curvature”, i.e., their TC is zero at one temperature and positive or negative at others
- Curvature arises from temperature variation of base-emitter voltages, collector currents, offset voltages
- Many curvature-correction techniques introduced in bipolar bandgap circuits, but rarely used in CMOS counterparts
- Samples of CMOS bandgap reference display substantially different zero-TC temperatures due to large offsets and process variations



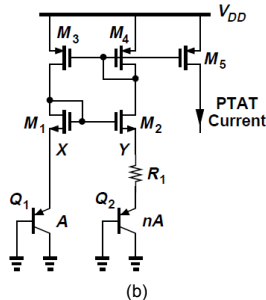 - PTAT currents can be generated by the topology shown in Fig. (a) below
- Alternatively, we can combine the supply-independent biasing scheme with a bipolar core, arriving at circuit in Fig. (b)
- Assume that  $M1-M2$  and  $M3-M4$  are identical pairs
- For  $ID1 = ID2$ , the circuit must ensure that  $VX = VY$
- Thus,  $ID1 = ID2 = (VT \ln n)/R1$ , yielding the same behavior for  $ID5$




## PTAT Current Generation


- A modified circuit to provide a bandgap reference voltage is shown below
- Idea is to add a PTAT voltage  $ID5R2$  to a base-emitter voltage; the output therefore equals

$$V_{REF} = |V_{BE3}| + \frac{R_2}{R_1} V_T \ln n$$

 - All PMOS transistors are assumed identical
- The value of  $V_{BE3}$  and size of  $Q3$  are somewhat arbitrary so long as their sum gives a zero TC



# Constant- $G_m$ biasing

 

- It is often desirable to bias transistors such that their transconductance does not depend on PVT
- Supply-independent bias topology shown can define the transconductance

- Bias current is given by

$$I_{out} = \frac{2}{\mu_n C_{ox} (W/L)_N} \frac{1}{R_S^2} \left(1 - \frac{1}{\sqrt{K}}\right)^2$$


- Thus, transconductance of  $M1$  equals

$$\begin{aligned} g_{m1} &= \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_N I_{D1}} \\ &= \frac{2}{R_S} \left(1 - \frac{1}{\sqrt{K}}\right), \end{aligned}$$

- If temperature coefficient of  $R_S$  is known, different techniques can cancel the temperature dependence
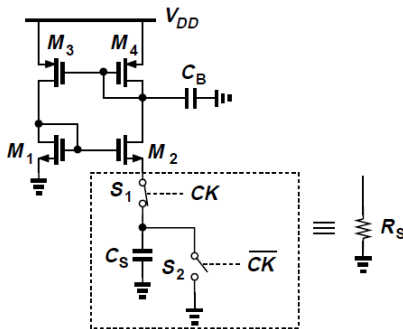
# Constant- $G_m$ biasing


- When a precise clock frequency is available,  $R_S$  can be replaced by a switched-capacitor equivalent for higher accuracy
- Average resistance of  $(CSf_{CK})^{-1}$  is established between source of  $M_2$  and ground, where  $f_{CK}$  is the clock frequency
- $CB$  shunts high-frequency components resulting from switching to ground





 
## Constant- $G_m$ biasing

- Switched-capacitor approach can be applied to other circuits as well
- As shown, a voltage-to-current converter with a relatively high accuracy can be constructed



 
# Speed and Noise Issues

- Reference generators are low-frequency circuits, but can impact speed of circuits they feed
- Various building blocks experience “crosstalk” through reference lines
- Caused by finite output impedance of reference generators
- In the configuration below, voltage at node  $N$  is heavily disturbed by circuit fed by  $M5$



 
# Speed and Noise Issues

- For fast changes in  $V_N$  the op amp cannot maintain  $V_P$  constant and bias currents of  $M_5$  and  $M_6$  experience large transient changes
- Duration of the transient at node  $P$  may be quite long if op amp has a slow response
- Reference generator may require a high-speed op amp




 
# Speed and Noise Issues

- For low-power applications, high-speed op amp may not be feasible
- Alternatively, node  $P$  in circuit below can be bypassed to ground by a large capacitor  $C_B$  to suppress external disturbances
- For stability of op amp to not degrade with addition of  $C_B$ , op amp must be of one-stage nature
- $C_B$  must be much greater than the capacitance that couples the disturbance to node  $P$



  
# Speed and Noise Issues

- As shown below, if  $C_B$  is not sufficiently large,  $V_P$  experiences a change and takes a long time to return to its original value, degrading the settling speed of circuits biased by reference generator [Fig. (a)]
- Preferable to leave node  $P$  agile
- In general, response of the circuit must be analyzed by applying a disturbance at the output and observing the settling behavior [Fig. (b)]



 
## Speed and Noise Issues

- Output noise of reference generators may impact the performance of low-noise circuits
- As shown below, load current source of a CS stage is driven by a bandgap circuit with a current multiplication factor of  $N$
- Thus, noise current of  $M1$  (or  $M2$ ) is multiplied by the same factor as it appears in  $M3$
- $M1$ - $M3$  carry noise due to the op amp  $A1$  as well


 
# Speed and Noise Issues


- As another example, if a high-precision A/D converter employs a bandgap reference voltage with which the analog input signal is compared, then the noise in the reference is directly added to the input


 
# Speed and Noise Issues

- As a simple example, let us calculate the output noise voltage of circuit below, considering only the input-referred noise voltage of the op amp,  $V_{n,op}$
- Since the small-signal drain currents of  $M1$  and  $M2$  are equal,  $V_{n,out}/(R_1 + g_{mN}^{-1})$ , we have  $V_P = -g_{mP}^{-1} V_{n,out}/(R_1 + g_{mN}^{-1})$ , obtaining the differential voltage at the input of the op amp as

$$-g_{mP}^{-1} A_0^{-1} V_{n,out}/(R_1 + g_{mN}^{-1})$$





# Speed and Noise Issues


- Beginning from node A, we can write

$$\frac{V_{n,out}}{R_1 + g_{mN}^{-1}} \cdot \frac{1}{g_{mN}} - \frac{V_{n,out}}{g_{mP} A_0 (R_1 + g_{mN}^{-1})} = V_{n,op} + V_{n,out}$$

- Hence,


$$V_{n,out} \left[ \frac{1}{R_1 + g_{mN}^{-1}} \left( \frac{1}{g_{mN}} - \frac{1}{g_{mP} A_0} \right) - 1 \right] = V_{n,op}$$

- Since typically  $g_{mP} A_0 \gg g_{mN} \gg R_1^{-1}$ ,  $|V_{n,out}| \approx V_{n,op}$
- Thus, noise of the op amp directly appears at the output

 

 
# Low-Voltage Bandgap References

- Bandgap voltage obtained previously is around 1.25 V, eluding implementation in today's supplies
- Fundamental limitation of addition of  $17.2VT$  to one  $V_{BE}$  to achieve a zero TC
- It may be possible to add two currents with positive and negative TCs and convert the result to an arbitrary voltage that has a zero TC
- We can readily generate a PTAT current given by  $VT \ln n/R$
- We need another current of the form  $V_{BE}/R$  with a negative TC



## Low-Voltage Bandgap References


- Returning to original bandgap circuit of Fig. (a), note that  $|I_{D4}| = VT \ln n/R1$  is a PTAT current
- Resistor  $R2$  is placed in parallel with  $Q2$
- $R1$  now carries an additional current of  $|V_{BE2}|/R2$ , i.e., a current with a negative TC
- PTAT behavior is now disturbed because  $I_{C1} \nparallel I_{C2}$

 

(a)


# Low-Voltage Bandgap References

- A simple modification as shown in Fig. (b) can solve this issue
- We tie  $R_2$  from  $Y$  to ground and place another resistor in parallel with  $Q_1$
- This topology lends itself to low-voltage implementation, requiring a minimum  $V_{DD}$  of  $V_{BE1} + |V_{DS3}|$

 

(b)

## Low-Voltage Bandgap References

 

- To analyze the circuit, we observe that  $V_X \approx V_Y \approx |V_{BE1}|$
- $I_{D3} = I_{D4}$

$$V_X \approx V_Y \approx |V_{BE1}| \mathbf{S}$$

$$I_{D3} = I_{D4}$$

- **This yields**  $I_{C1} + \frac{|V_{BE1}|}{R_3} = I_{C2} + \frac{|V_{BE1}|}{R_2}$ .

- We still have  $I_{C1} = I_{C2}$  and  $R_2 = R_3$

**We still have  
and hence**

$$|V_{BE1}| = |V_{BE2}| + I_{C2}R_1$$

$$I_{C2} = V_T \ln n / R_1$$

- This current and the current flowing through  $R_2$ ,  $|V_{BE1}|/R_2$ , constitute  $|I_{D4}|$ :


$$\begin{aligned} |I_{D4}| &= \frac{V_T \ln n}{R_1} + \frac{|V_{BE1}|}{R_2} \\ &= \frac{1}{R_2} \left( |V_{BE1}| + \frac{R_2}{R_1} V_T \ln n \right) \end{aligned}$$

# Low-Voltage Bandgap References

- Selecting  $(R_2/R_1)VT \ln n$  approximately equal to  $17.2VT$  renders a zero TC for  $ID_4$
- This current is then copied and passed through a resistor to generate a zero-TC voltage [Fig. (c)]:

$$V_{BG} = \frac{R_4}{R_2} \left( |V_{BE1}| + \frac{R_2}{R_1} V_T \ln n \right)$$

 
- We choose  $(R_2/R_1) \ln n \approx 17.2$ , observing that  $V_{BG}$  has a zero TC and its value can be lower than 1.25 V



(c)

# Low-Voltage Bandgap References


- Instructive to estimate the lowest supply voltage with which circuit of Fig. (c) can operate properly
- With large bipolar transistors and a small bias current, e.g., 10  $\mu\text{A}$ , the base-emitter voltage can be as low as 0.7 V
- Wide PMOS devices allow a  $|V_{DS}|$  of about 50 mV
- Minimum  $V_{DD}$  of 0.75 V is achievable
- In this case,  $R_4$  tends to be a large resistor, e.g., 50 k $\Omega$

 

(c)

## Low-Voltage Bandgap References

- The op amp can be realized as a five-transistor OTA
- OTA design guidelines:
  - (1) Large transistor dimensions to minimize flicker noise and offset
  - (2)  $V_{GS}$  of  $M_a$  and  $M_b$  plus headroom requires by  $I_{SS}$  must not exceed  $|V_{BE1}|$
  - (3) Transistors are chosen long enough to yield reasonable loop gain

 


(a)


 
## Low-Voltage Bandgap References

- Foregoing topology must include a start-up mechanism, else the circuit begins with  $V_X = V_Y = 0$ ,  $M_a$  and  $M_b$  remain off, and so do  $M_3$  and  $M_4$
- Since, with  $V_{DD} < 1$  V, the voltage difference between node  $P$  and node  $X$  is initially positive but finally negative, we can tie a diode-connected NMOS transistor between these two nodes to ensure start-up [Fig. (b)]
- Alternatively, it can be connected between  $X$  and  $V_{DD}$



(b)


# Low-Voltage Bandgap References

- Another low-voltage bandgap circuit can be derived by simply tying a resistor from the output to ground
- As shown, the circuit allows some of  $I_{D5}$  to flow through  $R_3$ :

$$|I_{D5}| = \frac{V_{out}}{R_3} + \frac{V_{out} - |V_{BE3}|}{R_2}$$


- If the PMOS devices are identical,  $|I_{D5}| = V_T \ln n / R_1$

$$V_{out} = \frac{R_3}{R_2 + R_3} \left( |V_{BE3}| + \frac{R_2}{R_1} V_T \ln n \right)$$

 

 
# Case Study

- We study a bandgap reference circuit designed for high-precision analog systems
- A simplified version of the core is shown below, with two series base-emitter voltages in each branch to reduce the effect of MOSFET mismatches
- PMOS current mirror ensures equal collector currents for  $Q1$ - $Q4$



 
# Case Study

- Channel-length modulation of MOS devices remains a significant issue
- To resolve this issue, each branch can employ both NMOS and PMOS cascode topologies
- Fig. (a) shows how the low-voltage cascode is utilized
- Fig. (b) shows a “self-biased” version




(a)

 


(b)

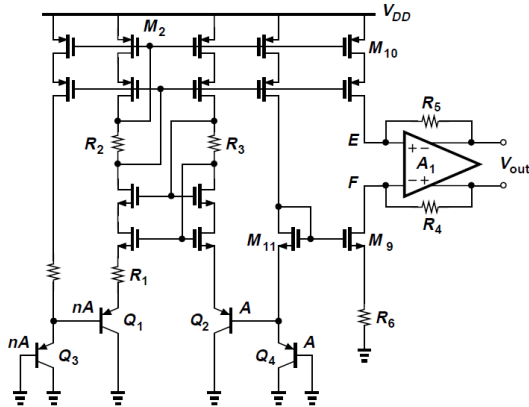- The bandgap circuit is designed to generate a floating reference, as shown in figure below
- $ID9$  and  $ID10$  flow through  $R4$  and  $R5$  respectively
- $M11$  sets the gate voltage of  $M9$  at  $V_{BE4} + V_{GS11}$ , establishing a voltage of  $V_{BE4}$  across  $R6$  if  $M9$  and  $M11$  are identical




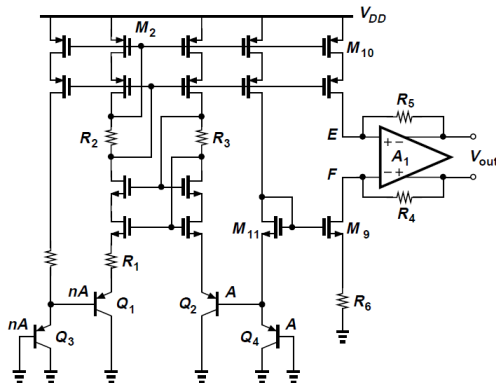- **Zero TC with proper choice of resistor ratios and  $n$**


 
# Case Study

- To enhance supply rejection, the design regulates the supply voltage of the core and the op amp
- Idea is to generate a local  $V_{DDL}$ , that is defined by a reference  $V_{R1}$  and the ratio of  $R_{r1}$  and  $R_{r2}$
- Remains relatively independent of the supply voltage



# Case Study

- To minimize dependence of  $VR1$  on the supply, it is established inside the core, as shown below
- $RM$  is chosen such that  $VR1$  is a bandgap reference

