

Chapter 16: Phase-Locked Loops

16.1 Simple PLL

16.2 Charge-Pump PLLs


16.3 Nonideal Effects in PLLs

16.4 Delay-Locked Loops

 16.5 Applications


Phase Detector (PD) Definition

- **PLL:** A feedback system that compares the output phase with the input phase.
- **Phase detector:** A circuit whose $\overline{V_{out}}$ is linearly proportional to the phase difference, $\Delta\phi$, between its two inputs:



- **KPD:** “Gain” of the PD = Slope of the line (V/rad).

XOR Gate as PD

 

- As $\Delta\phi$ varies, so does the width of the output pulses \square dc level proportional to $\Delta\phi$.
- XOR circuit produces error pulses on both rising and falling edges.
- Other PDs may respond only to positive or negative transitions.

Example 16.1

If output swing of the XOR = V_0 volts, what is the gain of a phase detector? Plot the input-output characteristics of the PD.


Solution:

- Gain = V_0/π .
- The input-output characteristics are plotted on the left:



- The average output voltage rises to $[V_0/\pi] \times \pi/2 = V_0/2$ for $\Delta\phi = \pi/2$ and V_0 for $\Delta\phi = \pi$.

- For $\Delta\phi > \pi$, the average begins to drop.

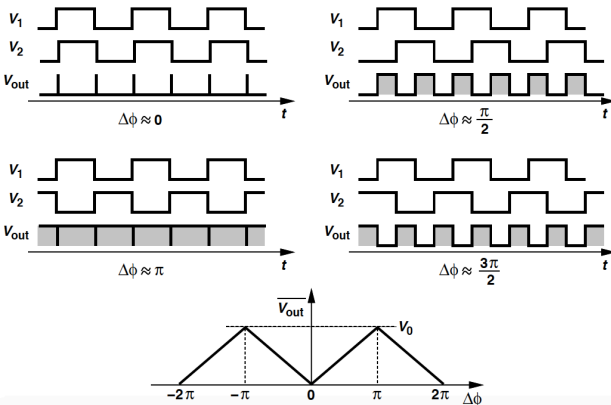- Periodic characteristic: Both negative and positive gains.



Skewed Waveforms Alignment

  


(a): Rising edges of V_{out} “skewed” by Δt seconds with respect to V_{CK} .

Assume the VCO has a single V_{cont} . To vary the phase, we must vary the frequency and allow $\phi = \int (\omega_0 + K_{VCO} V_{cont}) dt$.

(b): At $t = t_1$, the VCO frequency stepped to a higher value \square phase accumulated faster and phase error decreases $\square t = t_2$: phase error = 0.

PD & VCO in Feedback Loop

 - Output phase of a VCO can be aligned with phase of reference if
 - (1) frequency of the VCO is changed momentarily,
 - (2) a phase detector is used to determine when they are aligned.




(a)

 - Task of “phase locking”.
- (a): The PD compares the phase of V_{out} and V_{in} □ generates an error that varies the frequency until the phases are aligned.

Basic PLL Topology

- Topology (a) (Slide 6) must be modified because VPD
 - (1) consists of a dc component (desirable) & high-frequency components (undesirable),
 - (2) must be filtered as Vcont must remain quiet in the steady state.



(b)


- (b): Basic PLL topology.
- We define the loop of (b) to be locked if $\phi_{out} - \phi_{in}$ is constant:

$$\frac{d\phi_{out}}{dt} - \frac{d\phi_{in}}{dt} = 0 \quad \square \quad \omega_{out} = \omega_{in}.$$

Example 16.2


Implement a simple PLL in CMOS technology.

Solution

 

- Utilize an XOR gate as the phase detector.
- The VCO configured as a negative-Gm LC oscillator whose frequency is tuned by varactor diodes.


PLL Waveforms in Locked Condition

 

(a)

- (a): V_{in} & V_{out} exhibit a small phase difference but equal frequencies.
- PD: Pulses as wide as the skew between input & output.
- Low-pass filter extracts the dc component of V_{PD} □ apply result to the VCO (Assume gain of LPF = 1).
- “Ripple”: Small pulses in VLPF.

Calculation of Phase Error

 


- (b): VCO and PD characteristics.
- If input/output frequencies = ω_1 , the required V_{cont} is unique and = V_1 .
- Since $\omega_{out} = \omega_0 + K_{VCO}V_{cont}$ and

$$\overline{V_{PD}} = K_{PD}\Delta\phi \quad \square \quad \text{we can write:}$$

$$\text{and} \quad V_1 = \frac{\omega_1 - \omega_0}{K_{VCO}},$$
 
$$\begin{aligned} \phi_0 &= \frac{V_1}{K_{PD}} \\ &= \frac{\omega_1 - \omega_0}{K_{PD}K_{VCO}}. \end{aligned}$$





(b)

- Two important points:
 - Phase error varies as input frequency of the PLL varies.
 - To minimize phase error \square $K_{PD}K_{VCO}$ maximized.

Example 16.3

A PLL incorporates a VCO and a PD having the characteristics shown below. Explain what happens as the input frequency varies in the locked condition.


Solution

  

- PD characteristic is relatively linear near the origin but exhibits a small-signal gain of zero if $\Delta\phi = \pm\pi/2$, where the average output is equal to $\pm V_0$.
- If the input frequency is high enough ($= \omega_x$) to dictate $V_{cont} = V_0$, the PD must operate at the peak of its characteristic, at which, however, PD gain = 0 and the feedback loop fails.
- The circuit cannot lock if the input frequency reaches ω_x .


Equality of Input & Output Frequencies (I)

 - The exact equality of the input and output frequencies of a PLL in the locked condition is a critical attribute.
- Even a very small (deterministic) frequency error may prove unacceptable.
- E.g. (below): A data stream is to be processed synchronously by a clocked system. Even a slight difference between the data rate and the clock frequency results in a “drift” □ errors.




Equality of Input & Output Frequencies (II)

 - The equality would not exist if the PLL compared the input and output frequencies rather than phases.



(a)

 


(b)

- (a): A loop employing a FD would suffer from a finite difference between ω_{in} and ω_{out} due to various mismatches and other nonidealities.
- (b): An analogy with the unity-gain feedback circuit. Even if the op-amp's open-loop gain is infinity, the input-referred offset voltage leads to a finite error between V_{in} and V_{out} .

Response of PLL to Phase Step (I)

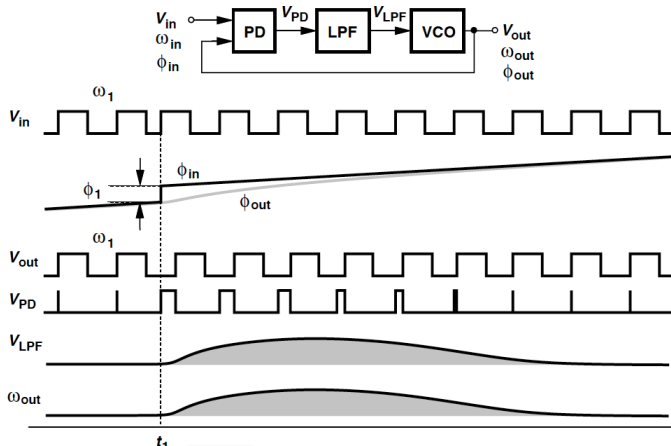- For a PLL in the locked condition, assume: $V_{in}(t) = V_A \cos \omega_1 t$
 $V_{out}(t) = V_B \cos(\omega_1 t + \phi_0)$
- The input experiences a phase step of ϕ_1 at $t = t_1$. The phase step manifests itself as a rising edge in V_{in} that occurs earlier (or later) than the periodicity would dictate.



Response of PLL to Phase Step (II)

- Output of the LPF does not change instantaneously \square the VCO initially continues to oscillate at ω_1 .
- The growing phase difference between input & output creates wide pulses at the output of PD \square force VLPF to rise.
- VCO frequency begins to change, to minimize the phase error.
- Then if the loop is to return to lock, ω_{out} eventually goes back to ω_1 \square VLPF & $\phi_{out} - \phi_{in}$ also returns to original values.
- The variation in the VCO frequency is such that:

$$\int_{t_1}^{\infty} \omega_{out} dt = \phi_1.$$


- \square when the loop settles, the output is:

$$V_{out}(t) = V_B \cos[\omega_1 t + \phi_0 + \phi_1 u(t - t_1)].$$

- \square ϕ_{out} gradually “catches up” with ϕ_{in} .


Response of PLL to Small Frequency Step

 - Examine the response of PLLs to $\Delta\omega$ at $t = t_1$:



- The VCO continues to operate at ω_1 immediately after t_1 .
 - PD generates increasingly wider pulses, VLPF rises with time.
- As $\omega_{out} \rightarrow \omega_1 + \Delta\omega$, the width of the pulses generated by the PD decreases, eventually settling to
- If the input frequency is varied slowly $(\omega_1 + \Delta\omega - \omega_0)/K_{VCO}$, tracks" ω_{in} .


Example of Phase Step Response

 

- At $t = t_2$, output frequency equals its final value, but the loop continues the transient because the phase error deviates from the required value.
- At $t = t_3$, the phase error is equal to its final value but the output frequency is not.
- For the loop to settle, both the phase and the frequency must settle to proper values.

Example 16.4 (I)

In the below PLL, V_{ex} is added to the output of the low-pass filter. (a) Determine the phase error and V_{LPF} if the loop is locked and $V_{ex} = V_1$. (b) Suppose V_{ex} steps from V_1 to V_2 at $t = t_1$. How does the loop respond?

 

Example 16.4 (II)

Solution

•(a) If the loop is locked, $\omega_{out} = \omega_{in}$, $V_{cont} = (\omega_{in} - \omega_0)/KVCO$.

□ $V_{LPF} = (\omega_{in} - \omega_0)/KVCO - V_1$, $\Delta\phi = V_{LPF}/KPD = (\omega_{in} - \omega_0)/(KPDKVCO) - V_1/KPD$.

•(b)


- When V_{ex} steps from V_1 to V_2 , V_{cont} immediately goes from $(\omega_{in} - \omega_0)/KVCO$ to $(\omega_{in} - \omega_0)/KVCO + (V_2 - V_1)$ □ change the VCO frequency to $\omega_{in} - KVCO(V_1 - V_2)$.

- V_{LPF} cannot change instantaneously □ PD begins to generate increasingly wider pulses, increasing V_{LPF} & ω_{out} .

- When the loop returns to lock, $\omega_{out} = \omega_{in}$, $V_{LPF} = (\omega_{in} - \omega_0)/KVCO - V_2$. Phase error also changes to $(\omega_{in} - \omega_0)/(KPDKVCO) - V_2/KPD$.

Change in the phase error:
$$\int_{t_1}^{\infty} \omega_{out} dt = \frac{V_1 - V_2}{K_{PD}}.$$

Variation of the Excess Phase with Time

 


(a)



(b)

- Assume the loop is initially locked and treat the PLL as a feedback system □ output quantity is the (excess) phase of the VCO.
- $\phi_{out}(s)/\phi_{in}(s)$: How the output phase tracks the input phase if the latter changes slowly or rapidly.
- $y_2(t)$ has faster phase variations than does $y_1(t)$.

Linear Model of Type I PLL (I)

 

- The overall PLL model consists of: Phase subtractor + LPF + VCO.
- In LPF transfer function, ω_{LPF} is -3-dB bandwidth.
- ϕ_{in} and ϕ_{out} : Excess phases of the input and output waveforms, respectively.

- Open-loop transfer function:
$$H(s)|_{open} = \frac{\Phi_{out}(s)|_{open}}{\Phi_{in}(s)|_{open}} = K_{PD} \cdot \frac{1}{1 + \frac{s}{\omega_{LPF}}} \cdot \frac{K_{VCO}}{s}$$

- Two poles: $s = -\omega_{LPF}$, $s = 0$. (“type I” system).

Linear Model of Type I PLL (II)

- **Close-loop transfer function:** $H(s)|_{\text{closed}} = \frac{K_{PD}K_{VCO}}{\frac{s^2}{\omega_{LPF}} + s + K_{PD}K_{VCO}}$
- If $s \rightarrow 0$, $H(s) \rightarrow 1$ because of the infinite loop gain. (Simply denote $H(s)|_{\text{closed}}$ by $H(s)$.)
- $H(s)$ also applies to:

$$\frac{\omega_{out}}{\omega_{in}}(s) = \frac{K_{PD}K_{VCO}}{\frac{s^2}{\omega_{LPF}} + s + K_{PD}K_{VCO}}$$

- If ω_{in} changes very slowly ($s \rightarrow 0$) \square ω_{out} tracks ω_{in} .
- If ω_{in} changes abruptly but the system is given enough time to settle ($s \rightarrow 0$) \square change in ω_{out} equals that in ω_{in} .
- We also have:

$$H(s) = K_{VCO} \cdot \frac{V_{cont}}{\omega_{in}}(s)$$

Linear Model of Type I PLL (III)


- Rewrite $H(s)$ as: $H(s) = \frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$
 - where “natural frequency”: $\omega_n = \sqrt{\omega_{LPF} K_{PD} K_{VCO}}$
 $\zeta = \frac{1}{2} \sqrt{\frac{\omega_{LPF}}{K_{PD} K_{VCO}}}$.
 - Two poles: $s_{1,2} = -\zeta\omega_n \pm \sqrt{(\zeta^2 - 1)\omega_n^2}$
- If $\zeta > 1$, real poles $= (-\zeta \pm \sqrt{\zeta^2 - 1})\omega_n$.
- If $\zeta < 1$, complex poles \Rightarrow response to $\omega_{in} = \Delta\omega u(t)$ is:

$$\omega_{out}(t) = \left\{ 1 - e^{-\zeta\omega_n t} [\cos(\omega_n \sqrt{1 - \zeta^2} t) + \frac{\zeta}{\sqrt{1 - \zeta^2}} \sin(\omega_n \sqrt{1 - \zeta^2} t)] \right\} \Delta\omega u(t)$$

- where $= [1 - \frac{1}{\sqrt{1 - \zeta^2}} e^{-\zeta\omega_n t} \sin(\omega_n \sqrt{1 - \zeta^2} t + \theta)] \Delta\omega u(t),$ (16.2)

$$\theta = \sin^{-1} \sqrt{1 - \zeta^2}$$

Underdamped Step Response of PLL

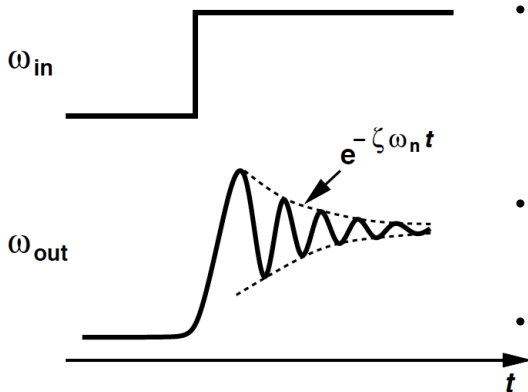

- The step response contains a sinusoidal component with frequency $\omega_n \sqrt{1 - \zeta^2}$ that decays with time constant $\cdot (\zeta \omega_n)^{-1}$
- To maximize settling speed of PLLS $\square \zeta \omega_n$ is maximized.
- Trade-off between the settling speed and the ripple on the VCO control line.

Example 16.5

Consider a 900-MHz PLL. $\omega_{LPF} = 2\pi \times (20 \text{ kHz})$. Output frequency changes from 901 MHz to 901.2 MHz. How long does it take to settle within 100 Hz of its final value?

Solution

•Step size = 200 kHz

$$\square \quad [1 - e^{-\zeta\omega_n t_s} \sin(\omega_n \sqrt{1 - \zeta^2} t_s + \theta)] \times 200 \text{ kHz} = 200 \text{ kHz} - 100 \text{ Hz}.$$

$$\square \quad e^{-\zeta\omega_n t_s} \sin(\omega_n \sqrt{1 - \zeta^2} t_s + \theta) = \frac{100 \text{ Hz}}{200 \text{ kHz}}.$$


•In the worse case, the sinusoid is unity and

•That is,

$$e^{-\zeta\omega_n t_s} = 0.0005.$$


$$\begin{aligned} t_s &= \frac{7.6}{\zeta\omega_n} \\ &= \frac{15.2}{\omega_{LPF}} \\ &= 0.12 \text{ ms}. \end{aligned}$$

Underdamped Step Response for Various ζ

 


- Severe ringing for $\zeta < 0.5$.
 - Trade-offs associated with choice of ζ :
 - Reduce ω_{LPF} to minimize ripple on V_{cont} ☐ stability degrades.
 - Lower phase error ☐ system less stable.
- (Phase error and ζ inversely proportional to $K_{PD}K_{VCO}$.)

Bode Plots of Type I PLL

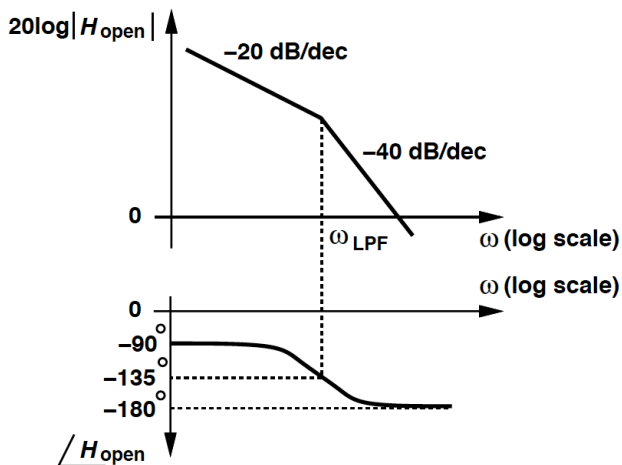


- A higher $K_{\text{PD}}K_{\text{VCO}}$ to minimize $\phi_{\text{out}} - \phi_{\text{in}}$ \square gain plot shifted up & gain crossover to the right \square phase margin degrades.
- The above is consistent with dependence of ζ upon $K_{\text{PD}}K_{\text{VCO}}$.

Root Locus of Type I PLL

 

- $K_{PD}K_{VCO} = 0$ \square loop is open, $\zeta = \infty$, and $s_1 = -\omega_{LPF}$, $s_2 = 0$.
- $K_{PD}K_{VCO}$ increases \square ζ drops and the two poles move toward each other on the real axis.
 - For $\zeta = 1$ (i.e., $K_{PD}K_{VCO} = \omega_{LPF}/4$), $s_1 = s_2 = -\zeta\omega_n = -\omega_{LPF}/2$.
- $K_{PD}K_{VCO}$ increases further \square two poles become complex with real part equal to $-\zeta\omega_n = -\omega_{LPF}/2$, moving in parallel with $j\omega$ axis.
- s_1 and s_2 moves away from the real axis \square system less stable.

PLL Transfer Function of Phase Error

 

- Another transfer function involves the error at the output of the phase subtractor:

$$H_e(s) = (\phi_{in} - \phi_{out}) / \phi_{in}$$

- $H_e(s)$ can be obtained by $\phi_{out} / \phi_{in} = H(s)$ and from

$$\begin{aligned} H_e(s) &= 1 - H(s) \\ &= \frac{s^2 + 2\zeta\omega_n s}{s^2 + 2\zeta\omega_n s + \omega_n^2} \end{aligned}$$

- As expected, $H_e(s) \rightarrow 0$ if $s \rightarrow 0$.

Example 16.6

A type-I PLL experiences a frequency step $\Delta\omega$ at $t = 0$. Calculate the change in the phase error.

Solution

• The Laplace transform of the frequency step = $\Delta\omega/s$.

• $\Phi_{in}(s) = (\Delta\omega/s)/s = \Delta\omega/s^2$

$$\square \quad \Phi_e(s) = H_e(s) \cdot \frac{\Delta\omega}{s^2}$$

$$= \frac{s^2 + 2\zeta\omega_n s}{s^2 + 2\zeta\omega_n s + \omega_n^2} \cdot \frac{\Delta\omega}{s^2}$$


\square For

$$\phi_e(t = \infty) = \lim_{s \rightarrow 0} s\Phi_e(s)$$

$$= \frac{2\zeta}{\omega_n} \Delta\omega$$

$$= \frac{\Delta\omega}{K_{PD}K_{VCO}}$$

Aided Acquisition

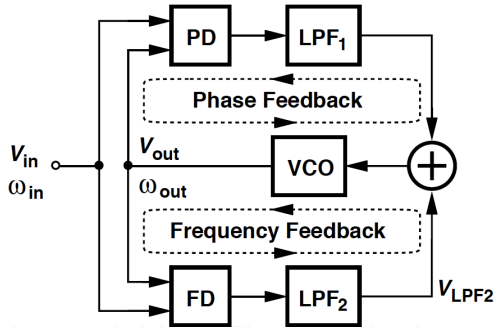


Problem of lock acquisition: The loop locks only if the difference between ω_{in} and ω_{out} is less than $\sim \omega_{LPF}$.

Aided acquisition:

- Compare ω_{in} and ω_{out} by frequency detector.
- Generate a dc component V_{LPF2} proportional to $\omega_{in} - \omega_{out}$
 - applied to VCO in a negative-feedback loop.
- Initially, FD drives ω_{out} toward ω_{in} , & PD output remains “quiet”.
- As $|\omega_{out} - \omega_{in}|$ sufficiently small □ PLL takes over □ Lock!

Phase/Frequency Detector (PFD)

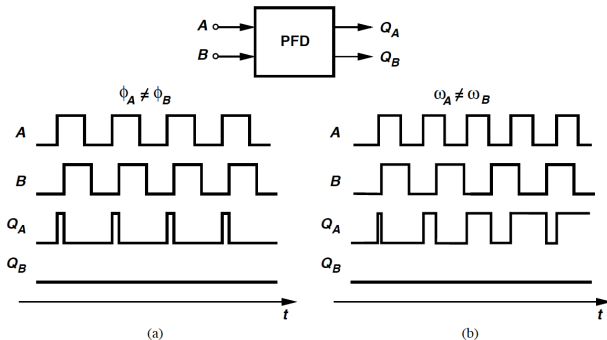


- If a rising edge on A followed by a rising edge on B \square Q_A goes high and returns to low, $Q_B = 0$. (Similar behavior for input B.)
- In (a), A leads B with equal frequencies \square Q_A continues to produce pulses with width proportional to $\phi_A - \phi_B$, $Q_B = 0$.
- In (b), A has a higher frequency & Q_A generates pulses, $Q_B = 0$.
- If A lags B or has a lower frequency than B \square Q_B produces pulses, $Q_A = 0$.
- Q_A : “UP” pulse, Q_B : “DOWN” pulse.

Example 16.7 (I)


Explain whether a master-slave D flipflop can operate as a phase detector or a frequency detector.

Solution


- In (a), first apply inputs with equal frequencies & finite phase difference.
- If A leads B \square V_{out} remains high indefinitely because flipflop continues to sample high levels of A.
- If A lags B \square V_{out} remains low.

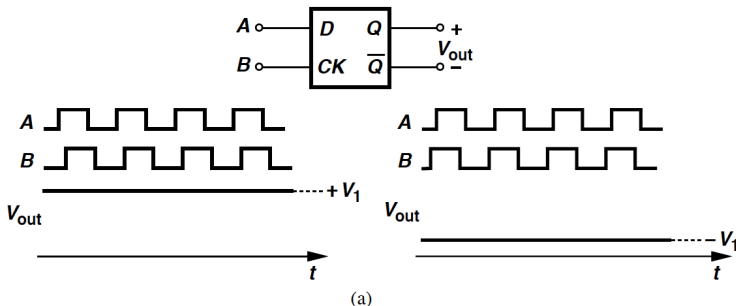

Example 16.7 (II)

 

 
- (b): High gain at $\Delta\phi = 0, \pm\pi, \dots$, zero gain at other $\Delta\phi$.
- D flipflop is called a “bang-bang” phase detector: The average value of V_{out} jumps from $-V_1$ to $+V_1$ as $\Delta\phi$ varies from 0^- to 0^+ .
- If the flipflop is to behave as a frequency detector, then average value of V_{out} has different polarities for $\omega_A > \omega_B$ & $\omega_A <$



- However, in (c), the average value of V_{out} is zero for both $\omega_A > \omega_B$ & $\omega_A < \omega_B$.

(c)

Implementation of PFD

 


- Simple implementation of PFD in (a): D inputs of two flipflops tied to logical ONE, A & B as clocks of the flipflops.
- If $Q_A = Q_B = 0$ & A goes high \square Q_A rises. Then if followed by rising on B \square Q_B goes high and the AND gate resets both flipflops.
- Each flipflop can be implemented as (b): Cross-coupled Latch 1 & Latch 2 respond to rising edges of CK and Reset, respectively.

Example 16.8


Determine the width of the narrow reset pulse that appear in the QB waveform in figure (a) (Slide 35).

Solution

 - (a) shown below illustrates the overall PFD at the gate level.
- If it begins with $A = 1$, $Q_A = 1$, and $Q_B = 0$, a rising edge on B forces $\overline{Q_B}$ to go low and, one gate delay later, Q_B to go high.
- In (b), this transition propagates to Reset, \overline{E} and \overline{F} , and finally to Q_A and Q_B .




(a)

 

(b)


- The width of the pulse on $Q_B \approx 5$ gate delays.

 Input-output Characteristic of 3-state PFD





- Define output as the difference between average values of QA and QB when $\omega_A = \omega_B$.
- The output varies symmetrically as $|\Delta\phi|$ begins from zero.
- For $\Delta\phi = \pm 360^\circ$, V_{out} reaches extrema and subsequently changes sign.
- Slope of this characteristic = gain.

PFD Followed by Low-Pass Filters

 

- The difference between average values of QA and QB is of interest □ Two outputs low-pass filtered and sensed differently.
- A PLL with such topology always locks.
- Suffers from a finite phase error due to finite KPFDVCO.

PFD with Charge Pump

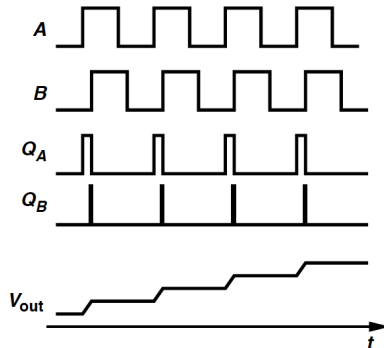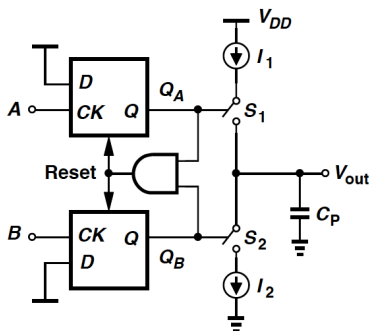


- To raise the loop gain to infinity, we first interpose a “charge pump” (CP) between PFD and loop filter.
- $Q_A = Q_B = 0$ \square S1 & S2 off, V_{out} remains constant.
- $Q_A = 1, Q_B = 0$ \square I1 charges CP.
- $Q_A = 0, Q_B = 1$ \square I2 discharges CP.
- E.g., A leads B \square QA continues to produce pulses, V_{out} rises steadily.

Example 16.9

What is the effect of the narrow pulses that appear in the QB waveform (Slide 39)?


Solution

 • QA and QB are simultaneously high for a finite period (Example 16.8) □ the current supplied by the charge pump to CP is affected.




- If $I_1 = I_2$, current through S1 simply flows through S2 during the narrow reset pulse □ no current to charge CP.
- Vout remains constant after QB goes high.

Basic Charge-Pump PLL

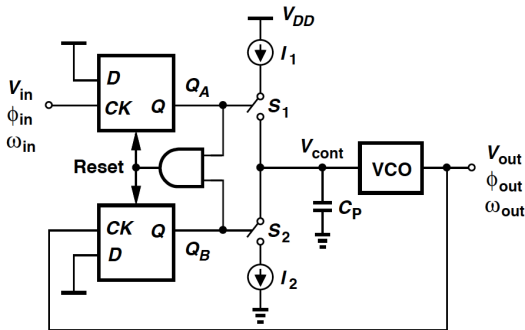

- **Charge-pump PLL:**
 - Senses transitions at input and output.
 - Detects phase/frequency differences.
 - Activates the charge pump accordingly.
- As ω_{out} approaches ω_{in} and when close enough \square PFD operates as phase detector, performing phase lock.
- When the loop is locked, V_{cont} is finite. \square Input phase error must be exactly zero (in contrast to type-I PLL).


Dynamics of CPPLL

 

- To test linearity of PFD/CP/LPF combination: Double input phase difference and see if V_{out} exactly doubles.
- The flat sections of V_{out} double but not the ramp sections.
- The current charging/discharging CP is constant ☐ constant slope for the ramp.
- Not linear in the strict sense.
- Approximate the output waveform by a ramp in (b) ☐ linear relationship between V_{out} and $\Delta\phi$.

Step Response of PFD/CP/LPF Combination

 - Assume input period = TD & charge pump provides $\pm I_P$ to the capacitor.
- Begin with zero phase difference, $\Delta\phi = \phi_0 u(t)$ \square QA or QB continues to produce pulses of $\phi_0 T_{in}/(2\pi)$ seconds wide.



- Approximated by a ramp \square
$$V_{out}(t) = \frac{I_P}{2\pi C_P} t \cdot \phi_0 u(t)$$

- The impulse response:
$$h(t) = \frac{I_P}{2\pi C_P} u(t)$$

\square Transfer function:

$$\frac{V_{out}}{\Delta\phi}(s) = \frac{I_P}{2\pi C_P} \cdot \frac{1}{s}$$

Example 16.10


Suppose the output quantity of interest in the circuit below is the current injected by the charge pump into the capacitor. Determine the transfer function from $\Delta\phi$ to this current, I_{out} .

Solution


• $V_{out}(s) = I_{out}/(C_P s)$

□
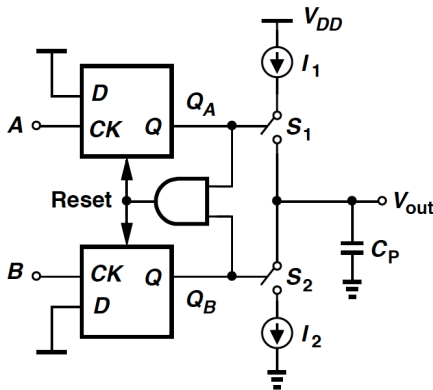
$$\frac{I_{out}}{\Delta\phi}(s) = \frac{I_P}{2\pi}.$$



Linear Model of Charge-pump PLL (I)


 


- The linear model of charge-pump PLLs has an open-loop transfer function: $\frac{\Phi_{out}}{\Phi_{in}}(s)|_{open} = \frac{I_P}{2\pi C_P} \frac{K_{VCO}}{s^2}$
- Loop gain has two poles at the origin □ “type II” PLL.
- Close-loop transfer function:


$$H(s) = \frac{\frac{I_P K_{VCO}}{2\pi C_P}}{s^2 + \frac{I_P K_{VCO}}{2\pi C_P}}$$

Linear Model of Charge-pump PLL (II)

  - $H(s)$ contains two imaginary poles at: $s_{1,2} = \pm j\sqrt{I_P K_{VCO} / (2\pi C_P)}$
☐ unstable system.
- In (a): constant total phase shift of 180° ☐ system oscillates at gain crossover frequency.
- To stabilize the system, phase shift $< 180^\circ$ at the gain crossover.
- (b): Accomplished by introducing a zero in loop gain, i.e., by adding a resistor in series with capacitor C_P .



Linear Model of Charge-pump PLL (III)

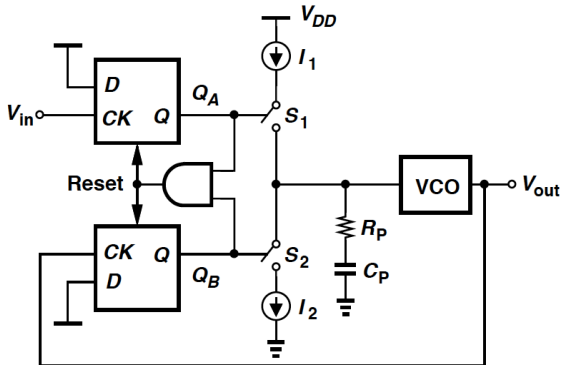

- In this circuit, transfer function of PFD/CP/LPF now becomes:

$$\frac{V_{out}(s)}{\Delta\phi} = \frac{I_P}{2\pi} \left(R_P + \frac{1}{C_P s} \right)$$

and

$$\frac{\Phi_{out}(s)}{\Phi_{in}(s)}|_{open} = \frac{I_P}{2\pi} \left(R_P + \frac{1}{C_P s} \right) \frac{K_{VCO}}{s}$$

□


$$H(s) = \frac{\frac{I_P K_{VCO}}{2\pi C_P} (R_P C_P s + 1)}{s^2 + \frac{I_P}{2\pi} K_{VCO} R_P s + \frac{I_P}{2\pi C_P} K_{VCO}}$$

- Close-loop system contains a zero at $s_z = -1/(R_P C_P)$.

- Using the same notation as before, we have: $\omega_n = \sqrt{\frac{I_P K_{VCO}}{2\pi C_P}}$

$$\zeta = \frac{R_P}{2} \sqrt{\frac{I_P C_P K_{VCO}}{2\pi}}$$

Charge-pump PLL: Stability Issues

 

In Bode plots of the loop gain:
 IPKVCO decreases \square gain crossover frequency moves toward the origin \square phase margin degrades.

In root locus of the close-loop system in complex plane:


- IPKVCO = 0 \square loop open, both poles at the origin
- IPKVCO > 0 \square $s_{1,2} = -\zeta\omega_n \pm \omega_n\sqrt{\zeta^2 - 1}$
- Complex poles if IPKVCO is small.
- IPKVCO increases \square s_1, s_2 move on a circle centered $\sigma = -1/(R_P C_P)$ & radius = $1/(R_P C_P)$
- For $\zeta \geq 1$, poles are real.
- For complex s_1, s_2 , $\zeta = \cos\psi$:
 IPKVCO exceeds zero \square more stable.

Example 16.11


Explain the flaw: A student considers the Bode plots and observes that at ω_1 , the loop gain > 1 & phase shift $= -180^\circ$. Then the PLL must oscillate at this frequency.

Solution

 - The phase shift is in fact slightly less than zero unless $\omega' = 0$.
- Using Nyquist's approach (Chapter 10), a system containing two integrators and one zero does not oscillate.




Charge-pump PLL: Addition of C2

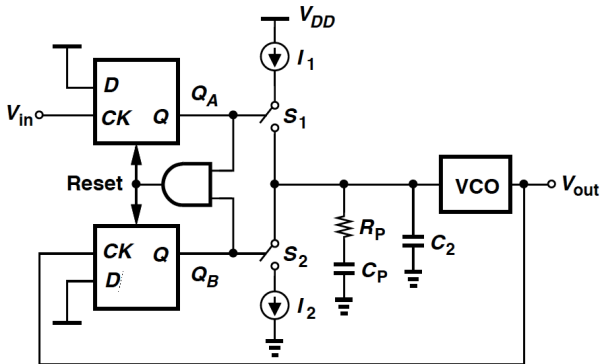

- For the compensated type-II PLL: V_{cont} experiences large jump \square disturb VCO.
- A second capacitor added in parallel with R_P and C_P \square suppress the initial step.
- Third-order PLL. If C_2 is about 1/5 to 1/10 of C_P \square close-loop time and frequency responses remain relatively unchanged.
- In reality, R_P becomes very large \square stability degrades again.


PFD/CP Nonidealities

 


If A & B rise simultaneously, so do Q_A & Q_B □ activate reset.

(a): A hypothetical PFD that produces no pulses for a zero input phase difference.

 (b): The circuit generates very narrow pulses on Q_A or Q_B .




(a)

 


(b)

Dead Zone in Charge Pump Current

 



- If $\Delta\phi$ falls below ϕ_0 \square output voltage of PFD/CP/LPF combination is no longer a function of $\Delta\phi$.
- For $|\Delta\phi| < \phi_0$, charge pump injects no current \square loop gain drops to zero and output phase is not locked.
- Thus PFD/CP circuit suffers from a dead zone equal to $\pm\phi_0$ around $\Delta\phi = 0$.

Jitter from Dead Zone

 


- Dead zone allows VCO to accumulate as much random phase error as ϕ_0 with respect to input while receiving no corrective feedback.
- The zero crossing points of the VCO output experience substantial random variations \square “jitter.”

  Response of Actual PD to a small $\Delta\phi$




- The coincident pulses on QA and QB can eliminate dead zone.
- An infinitesimal increment in $\Delta\phi$ \propto proportional increase in net current produced by the charge pump.


Effect of Skew

 

(a)

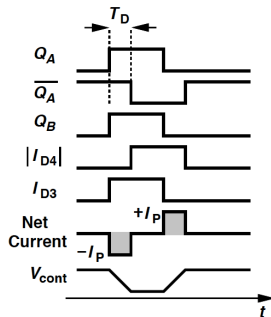


(b)

 

(c)


- (a): M1 & M2 as Current sources, M3 & M4 as Switches. Output QA is inverted. QA goes high \square M4 turns on.
- Issue of (a): As in (b), net current injected by the charge pump into loop filter jumps to $+I_P$ & $-I_P$ \square disturb V_{cont} periodically.
- (c) can equalize the delays and suppress the above effect.

Effect of UP & DOWN Current Mismatch

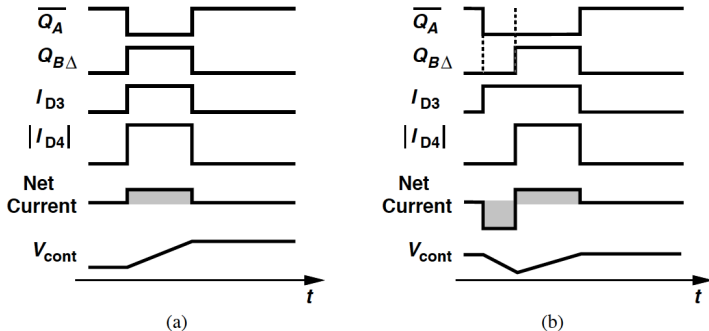


- (a): Even with perfect alignment of UP & DOWN pulses, net current $\neq 0$ \square charge V_{cont} by a constant increment at each phase comparison instant.
- For the loop to remain locked, average value of V_{cont} must remain constant \square (b): PLL creates a phase error between input & output such that net current in every cycle = 0.


Charge Sharing between CP, CX & CY

 

(a)

 


(b)

 


- Suppose in (a), S1 & S2 off \square M1 discharge X to ground, M2 charge Y to VDD.
- (b): Next phase comparison instant, both S1 & S2 on \square VX rises, VY falls, $VX \approx VY \approx V_{cont}$.
- Even if $CX = CY$, change in VX is not equal to that in VY \square difference between the two changes must be supplied by CP \square a jump in Vcont.

Bootstrapping

 


- Charge sharing can be suppressed by “bootstrapping.”
- When S_1 & S_2 off, S_3 & S_4 on \square allow unity-gain amplifier to hold V_X & V_Y at V_{cont} .
- Next phase comparison instant, S_1 & S_2 on, S_3 & S_4 off \square V_X & V_Y begin with V_{cont} \square no charge sharing between C_P and capacitances at X & Y.

Ideal vs. Jittery Waveforms

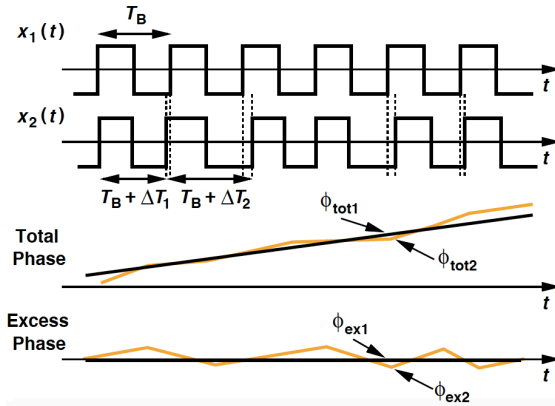


- Strictly periodic $x_1(t)$ contains zero crossings evenly spaced in time.
- Nearly periodic $x_2(t)$ displaces zero crossings from ideal points.
- We say $x_2(t)$ suffers from jitter.
- From plots of ϕ_{out} and ϕ_{ex} , jitter manifests itself as variation of ϕ_{ex} with time.

Slow vs. Fast Jitter

 

- $y_1(t)$: instantaneous frequency varies slowly from one period to the next \square “slow jitter.”
- $y_2(t)$: “fast jitter.”
- Rate of change is also evident from ϕ_{ex} plots of the two waveforms.
- Slow jitter at input propagates to output unattenuated but fast jitter does not.

Effect of VCO Jitter


 


- Suppose input is strictly periodic but VCO suffers from jitter.
- In this model, $x_{in}(t) = A \cos \omega t$, a random component Φ_{VCO} is added to the output of VCO to represent its jitter.

□ For type-II PLL:
$$\frac{\Phi_{out}}{\Phi_{VCO}}(s) = \frac{s^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$


- The characteristic has a high-pass nature □ slow jitter components generated by VCO are suppressed but fast jitter components are not.

  Response of PLL to Input Jitter & VCO Jitter




- Depending on the application and the application, one or both sources (input jitter & VCO jitter) may be significant, requiring an optimum choice of the loop bandwidth.

Generation of Clock Edges

 


(a)

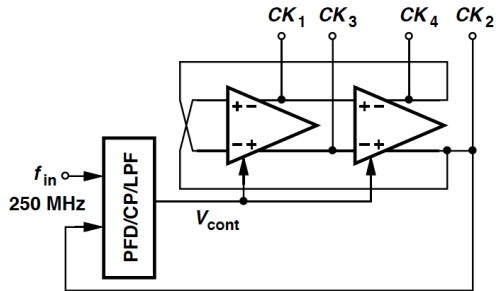


(b)

- (a): Four clock phases with $\Delta T = 1\text{ ns}$ between consecutive edges.
- (b): To generate phases in (a), use a two-stage differential ring oscillator, locked to a 250-MHz reference \square output period is exactly 4 ns .

Simple Delay-Locked Loop (DLL)

 

(a)

 


(b)

- (a) also generates the clock phases (Slide 63): Apply input clock to four delay stages in a cascade.
 - Does not produce a well-defined edge spacing.
- (b): Simple delay-locked loop (incorporates VCDL not a VCO)
 - Phase difference between CK_{in} and CK_4 sensed by a PD.
 - A proportional average voltage, V_{cont} , generated.
 - Delay adjusted with negative feedback.
 - Large loop gain \square small phase difference between CK_{in} & CK_4
 - \square establish precise edge spacing.

 Example 16.12

Explain qualitatively what type of transfer function the DLL shown below has.



Solution

•For slow phase fluctuations on input:

- Phase error sees a high gain through PD/CP/LPF.
- Delay of the line is adjusted so as to minimize this error.

□ ϕ_{out} tracks ϕ_{in} , gain is about unity.


•For very fast phase changes on input:

- Feedback loop has little gain, V_{cont} relatively constant.
- Input phase variations directly propagates to output


□ gain of about unity.

•The DLL exhibits all-pass response, but the response may have a dip or a peak for moderately fast phase changes.

Frequency Multiplication

 

(a)

 

(b)


- (a) **Voltage amplification:** A feedback system amplifies V_{in} by a factor M if $R_2/(R_1 + R_2) = 1/M$, and compare the result with V_{in} .
- (b) **Frequency multiplication:** f_{out} of a PLL divided by M and applied to the phase detector $\square f_{out} = Mf_{in}$.

- Rewrite the equation on Slide 50 as:

$$\begin{aligned}
 H(s) &= \frac{\frac{I_P}{2\pi} \left(R_P + \frac{1}{C_P s} \right) \frac{K_{VCO}}{s}}{1 + \frac{1}{M} \frac{I_P}{2\pi} \left(R_P + \frac{1}{C_P s} \right) \frac{K_{VCO}}{s}} \\
 &= \frac{\frac{I_P K_{VCO}}{2\pi C_P} (R_P C_P s + 1)}{s^2 + \frac{I_P K_{VCO}}{2\pi C_P} R_P s + \frac{I_P K_{VCO}}{2\pi C_P} \frac{1}{M}}
 \end{aligned}$$


- Compare the denominators of two equations of $H(s)$ \square frequency division in the loop manifests itself as division of K_{VCO} by M .

VCO/Divider combination

 



- For the VCO/divider cascade, we have:
$$\begin{aligned}\omega_{out} &= \frac{\omega_0 + K_{VCO} V_{cont}}{M} \\ &= \frac{\omega_0}{M} + \frac{K_{VCO}}{M} V_{cont}\end{aligned}$$
- This combination is equivalent to a VCO with an intercept frequency = ω_0/M and gain = K_{VCO}/M .
- Then we can rewrite:
$$\omega_n = \sqrt{\frac{I_P}{2\pi C_P} \frac{K_{VCO}}{M}}$$
$$\zeta = \frac{R_P}{2} \sqrt{\frac{I_P C_P}{2\pi} \frac{K_{VCO}}{M}}.$$
- Decay time constant is: $(\zeta \omega_n)^{-1} = 4\pi M / (R_P I_P K_{VCO})$ and settling speed.

Phase-Locked Frequency Synthesizer

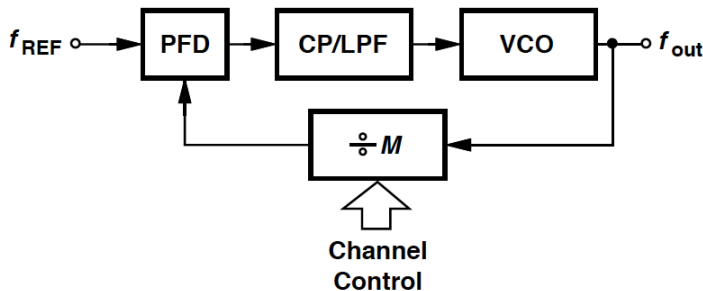


- **Channel control input:** A digital word that defines value of M .
- **$f_{out} = Mf_{REF}$,** the relative accuracy of f_{out} is equal to that of f_{REF} .
- **f_{REF} derived from a stable, low-noise oscillator.**

Skew between Data and Buffered Clock

  

- A synchronous pair of data and clock lines enter a large digital chip.
- The clock typically drives a large number of transistors and long interconnects \square be the first applied to a large buffer.
- The clock distributed on the chip may suffer from substantial skew, ΔT , with respect to the data.

Use of PLL to Eliminate Skew

 

- An CK_{in} is applied to an on-chip PLL and the buffer is placed inside the loop.
- The PLL guarantees a nominally-zero phase difference between CK_{in} and CK_B \square skew is eliminated.
- Constant phase shift introduced by buffer is divided by infinite loop gain of the feedback system.


Example 16.13

Construct the voltage-domain counterpart of the loop (Slide 70).

Solution

- The buffer creates a constant phase shift in the signal generated by VCO.

 □ **voltage-domain counterpart assumes the below topology:**




- We have:

$$(V_{in} - V_{out})A + V_M = V_{out} \quad \square \quad V_{out} = \frac{AV_{in} + V_M}{1 + A}.$$

- As $A \rightarrow \infty$, $V_{out} \rightarrow V_{in}$.

Jitter Reduction

 

- **Jittery waveforms:** Typically “retimed” by a low-noise clock.
- **(a):** Resample the midpoint of each bit by a D flipflop driven by the clock.
 - However the clock may not be available independently.
- **Modified as (b):** A “clock recovery circuit” (CRC) produces clock from the data.
 - minimize effect of input jitter on the recovered clock.