

# Quiz 04 Basic Components

總分 100/100 ?

NCTU EELAB Fall

區段分數 0/0

Class \*

☐ DEE222☒ DEE320

Student ID \*

0710175

Name \*

陳愉方

## Q1. Answer the following questions about capacitors.

區段分數 20/20



✓ (1) Mark the polarity of capacitor below. \*

5/5




- ☒ X : high potential , Y : low potential
- ☐ X : low potential , Y : high potential
- ☐ There is no difference between X and Y pins.

✓

✓ (2) Following the previous question, look at the circuit below, how should you connect the capacitor between node A and B? \*

5/5

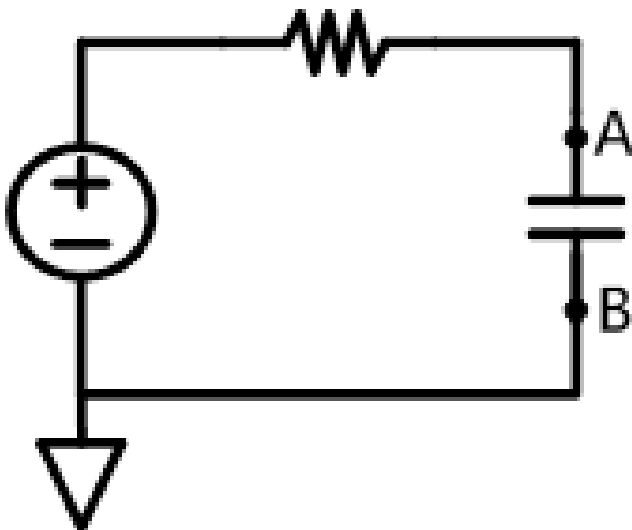

- ☒ X-A , Y-B
- ☐ X-B , Y-A
- ☐ Both ways is ok.

✓

(3) According to the capacitance code, identify the value of capacitors a and b.

## Capacitance code

- Two-digit magnitude plus one exponential digit in the unit of pF (p = pico =  $10^{-12}$ )
  - **106** -> **10** x  $10^6$  pF = 10  $\mu$ F
  - **050** -> **5** x  $10^0$  pF = 5 pF
  - **Exception 1: only two digits; 47 -> 47 pF**
  - **Exception 2: code with a round point 6.8 -> 6.8  $\mu$ F**



✓ a. \*

5/5



- ☐ 5  $\mu$ F
- ☐ 0.5  $\mu$ F
- ☒ 0.05  $\mu$ F



✓ b \*

5/5

☐ 4.7 pF☒ 4.7 μF☐ 47 μF

✓


Q2. Answer the following questions about inductors.

區段分數 30/30




HINT

# How to read the inductance

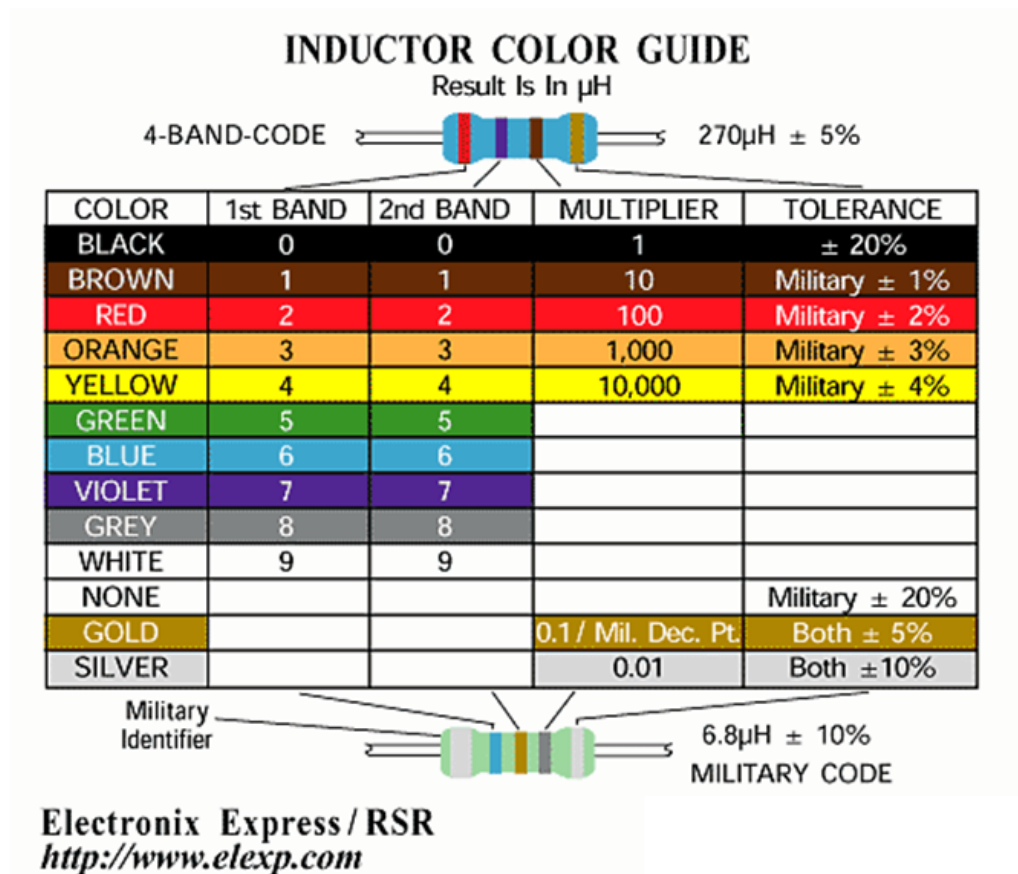

✓ (1) According the color code, identify the value of inductor. 15/15

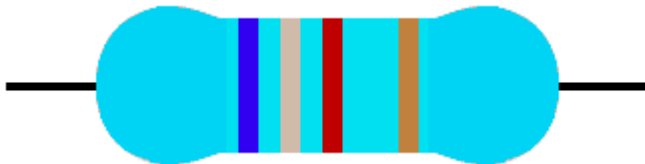\*colors from left to right : blue . grey . red . gold \*



- ☐ 6.8  $\mu\text{H} \pm 5\%$
- ☐ 680  $\mu\text{H} \pm 5\%$
- ☒ 6.8 mH  $\pm 5\%$

✓

✓ (2) Given a 1 mH inductor with 5% error, what is the color code? \*

15/15




- ☐ (a , b , c) = (black , brown , orange)
- ☐ (a , b , c) = (black , brown , red)
- ☐ (a , b , c) = (brown , black , black)
- ☒ (a , b , c) = (brown , black , red)



Q3. In Lab4, we'll do the experiments about basic RC and RL circuits, try to match the corresponding diagrams and formulas respectively.

區段分數 50/50

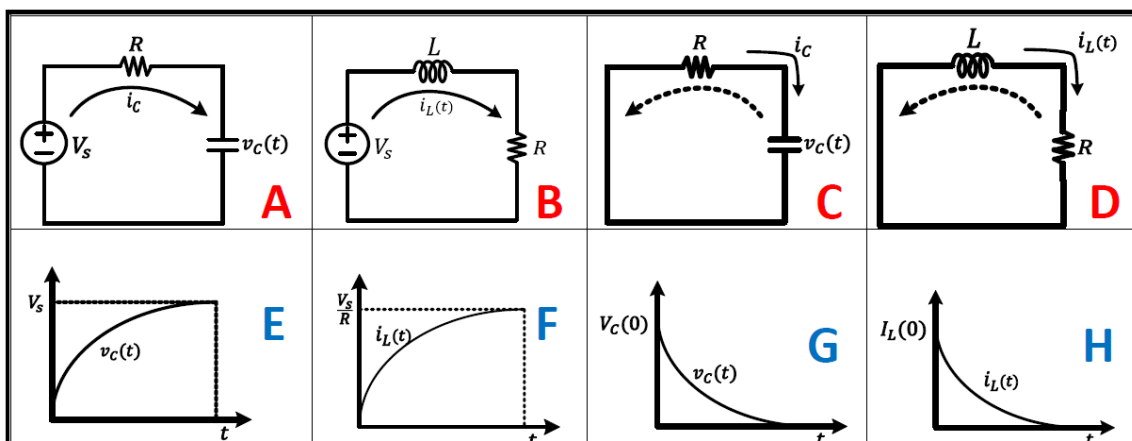

I $v_C(t) = V_s(1 - e^{-t/RC})$	J $v_C(t) = V_C(0)e^{-t/RC}$	K $i_L(t) = \frac{V_s}{R}(1 - e^{-\frac{R}{L}t})$	L $i_L(t) = I_L(0)e^{-\frac{R}{L}t}$
---------------------------------	------------------------------	---	--------------------------------------

✓ (1) Find the diagrams and formulas of RC circuit in charging state. \*

- ☒ A ✓
- ☐ B
- ☐ C
- ☐ D
- ☒ E ✓
- ☐ F
- ☐ G
- ☐ H
- ☒ I ✓
- ☐ J
- ☐ K
- ☐ L



✓ (2) Find the diagrams and formulas of RC circuit in discharging state. \*

10/10

☐ A☐ B☒ C

✓

☐ D☐ E☐ F☒ G

✓

☐ H☐ I☒ J

✓

☐ K☐ L



✓ (3) Find the diagrams and formulas of RL circuit in charging state. \* 10/10

☐ A

☒ B

✓

☐ C

☐ D

☐ E

☒ F

✓

☐ G

☐ H

☐ I

☐ J

☒ K

✓

☐ L



✓ (4) Find the diagrams and formulas of RL circuit in discharging state. \* 10/10

☐ A

☐ B

☐ C

☒ D

✓

☐ E

☐ F

☐ G

☒ H

✓

☐ I

☐ J

☐ K

☒ L

✓

✓ (5) Given  $R=1\text{ k}\Omega$  ,  $C=0.05\text{ }\mu\text{F}$  ,  $L=1\text{ mH}$ , calculate the closest answers of time constant  $\tau_{RC}$  and  $\tau_{RL}$ . \* 10/10

☐ ( $\tau_{RC}$  ,  $\tau_{RL}$ ) = (50 ps , 1  $\mu\text{s}$ )

☐ ( $\tau_{RC}$  ,  $\tau_{RL}$ ) = (50  $\mu\text{s}$  , 1 s)

☒ ( $\tau_{RC}$  ,  $\tau_{RL}$ ) = (50  $\mu\text{s}$  , 1  $\mu\text{s}$ )

✓



這份表單是在 國立交通大學 中建立。 - [服務條款](#)

Google 表單

