

老師說電考題：

已知 (2.25) 式, $V_1 = |V_1| e^{j\theta_1}$, $V_2 = |V_2| e^{j\theta_2}$
 $Z = R + j\omega L = |Z| e^{j\angle Z}$, $\theta_{12} = \theta_1 - \theta_2$

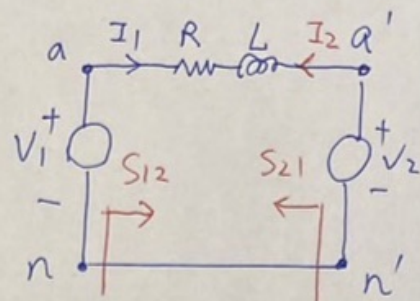


圖 2.14 單相電路

可推導 (2.26) $S_{12} = V_1 \cdot I_1^*$, 因為 $I_1 = \frac{V_1 - V_2}{Z}$

$$S_{12} = V_1 \cdot \left(\frac{V_1 - V_2}{Z} \right)^* = \frac{V_1 \cdot V_1^* - V_1 \cdot V_2^*}{Z^*}$$

$$= \frac{|V_1|^2 - |V_1| \cdot |V_2| e^{j\theta_{12}}}{|Z| \cdot e^{-j\angle Z}} = \frac{|V_1|^2}{|Z|} \cdot e^{j\angle Z} - \frac{|V_1| |V_2|}{|Z|} e^{j\angle Z} \cdot e^{j\theta_{12}}$$

可推導 (2.27) $S_{21} = V_2 \cdot I_2^*$, 因為 $I_2 = \frac{V_2 - V_1}{Z}$

$$S_{21} = V_2 \cdot \left(\frac{V_2 - V_1}{Z} \right)^* = \frac{|V_2|^2}{|Z|} \cdot e^{j\angle Z} - \frac{|V_2| |V_1|}{|Z|} \cdot e^{j\angle Z} \cdot e^{-j\theta_{12}}$$

所以 (2.28) $-S_{21} = -\frac{|V_2|^2}{|Z|} \cdot e^{j\angle Z} + \frac{|V_2| |V_1|}{|Z|} \cdot e^{j\angle Z} \cdot e^{-j\theta_{12}}$

(2.29) $S_{12} = C_1 - B e^{j\theta_{12}}$, (2.30) $-S_{21} = C_2 + B e^{-j\theta_{12}}$

送端圓圓心 $C_1 = \frac{|V_1|^2}{|Z|} e^{j\angle Z}$, 受端圓圓心 $C_2 = -\frac{|V_2|^2}{|Z|} e^{j\angle Z}$, 半徑 $B = \frac{|V_1| |V_2|}{|Z|} e^{j\angle Z}$

簡化, 假設 $R=0$, $Z = j\omega L = jX \Rightarrow |Z| = X$, $\angle Z = 90^\circ$, 代入 (2.26) 和 (2.27)

(2.26) $S_{12} = \frac{|V_1|^2}{|Z|} \cdot (\cos 90^\circ + j \sin 90^\circ) - \frac{|V_1| |V_2|}{|Z|} \cdot (\cos 90^\circ + j \sin 90^\circ) \cdot (\cos \theta_{12} + j \sin \theta_{12})$
 $= j \frac{|V_1|^2}{X} - j \frac{|V_1| |V_2|}{X} \cos \theta_{12} + \frac{|V_1| |V_2|}{X} \sin \theta_{12} = P_{12} + j Q_{12}$

所以實功 $P_{12} = \frac{|V_1| |V_2|}{X} \sin \theta_{12}$ (2.31), $Q_{12} = \frac{|V_1|^2}{X} - \frac{|V_1| |V_2|}{X} \cos \theta_{12}$ (2.32)

(2.27) $S_{21} = \frac{|V_2|^2}{|Z|} \cdot (\cos 90^\circ + j \sin 90^\circ) - \frac{|V_2| |V_1|}{|Z|} \cdot (\cos 90^\circ + j \sin 90^\circ) \cdot (\cos(-\theta_{12}) + j \sin(-\theta_{12}))$
 $= j \frac{|V_2|^2}{X} - j \frac{|V_1| |V_2|}{X} \cos \theta_{12} - \frac{|V_1| |V_2|}{X} \sin \theta_{12} = P_{21} + j Q_{21}$

所以實功 $P_{21} = -\frac{|V_1| |V_2|}{X} \sin \theta_{12} = -P_{12}$


$Q_{21} = \frac{|V_2|^2}{X} - \frac{|V_2| |V_1|}{X} \cos \theta_{12}$ (2.33)

考考：

例 2.14 如圖系統中所有的值都是單相值

(a) 選取 Q_{G2} 使得 $|V_2| = 1$ (b) 此時 $\angle V_2$ 是多少？

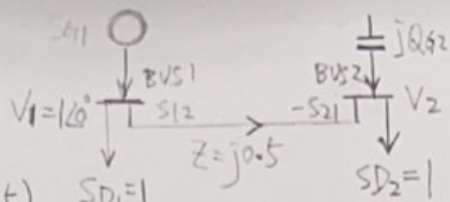當 Bus1 和 Bus2 的傳輸線上只有電抗 $z = j0.5$ 時, ($X = 0.5$) $SD_1 = 1$



(2.31) 實功 $P_{12} = -P_{21} = \frac{|V_1||V_2|}{X} \sin \theta_{12}$, 因為流進 Bus2 的實功等於流出的實功

所以 $P_{12} = SD_2 = 1 = \frac{1 \times 1}{0.5} \sin \theta_{12} \Rightarrow \sin \theta_{12} = 0.5 \Rightarrow \theta_{12} = 30^\circ \Rightarrow \angle V_2 = -30^\circ$

$$(2.32) Q_{12} = \frac{|V_1|^2}{X} - \frac{|V_1||V_2|}{X} \cos \theta_{12}$$

$$(2.33) Q_{21} = \frac{|V_2|^2}{X} - \frac{|V_1||V_2|}{X} \cos \theta_{12}$$

因為流進 Bus2 的虛功等於流出的虛功

所以 $Q_{G2} = Q_{21} = \frac{|V_2|^2}{X} - \frac{|V_1||V_2|}{X} \cos \theta_{12}$ (已知 $|V_1| = 1, |V_2| = 1, X = 0.5, \theta_{12} = 30^\circ$)

$$= 2 - 2 \cos 30^\circ = 0.268, Q_{G2} > 0 \text{ 相當於電容器電源}$$

(c) 如果 $Q_{G2} = 0$, 能供應負載 SD_2 嗎? (d) 如果能, V_2 又是多少?

已知 $|V_1| = 1, X = 0.5$, 未知 $V_2 = ?$, $\theta_{12} = ?$

$$\text{由 (2.31)} P_{12} = -P_{21} = \frac{|V_1||V_2|}{X} \sin \theta_{12} = 2|V_2| \sin \theta_{12} = SD_2 = 1 \quad \text{--- ①}$$

$$\text{由 (2.33)} Q_{G2} = 0 = Q_{21} = \frac{|V_2|^2}{X} - \frac{|V_1||V_2|}{X} \cos \theta_{12} = 2|V_2|^2 - 2|V_2| \cos \theta_{12} \quad \text{--- ②}$$


由 ① 可得 $\sin \theta_{12} = \frac{1}{2|V_2|}$, 由 ② 可得 $\cos \theta_{12} = |V_2|$

$$\text{所以 } \sin \theta_{12} = \frac{1}{2 \cos \theta_{12}} \Rightarrow 2 \sin \theta_{12} \cos \theta_{12} = 1 \Rightarrow \sin 2\theta_{12} = 1$$

$$\Rightarrow 2\theta_{12} = 90^\circ \Rightarrow \theta_{12} = 45^\circ$$

$$\Rightarrow |V_2| = \cos \theta_{12} = \frac{1}{\sqrt{2}}$$
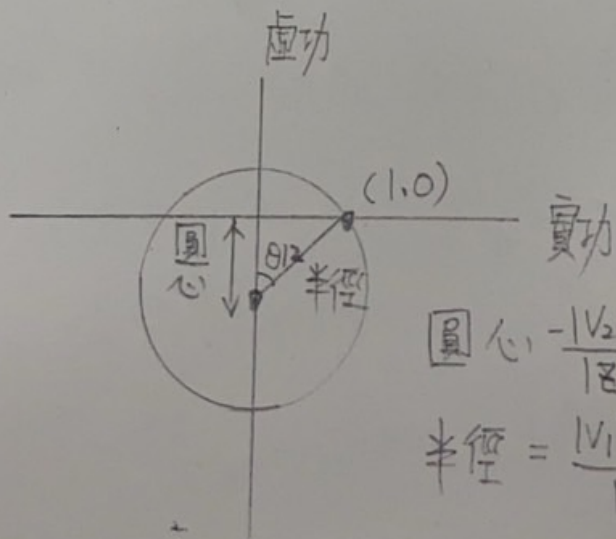
$$\Rightarrow V_2 = 0.707 \angle -45^\circ$$



$$\text{圓心 } -\frac{|V_2|^2}{|Z|} = -2|V_2|^2, \text{ 絕對值 } 2|V_2|^2$$

$$\text{半徑} = \frac{|V_1||V_2|}{|Z|} = 2|V_2|$$

已知 (2.25) 式, $V_1 = |V_1| e^{j\theta_1}$, $V_2 = |V_2| e^{j\theta_2}$
 $Z = R + j\omega L = |Z| e^{j\angle Z}$, $\theta_{12} = \theta_1 - \theta_2$

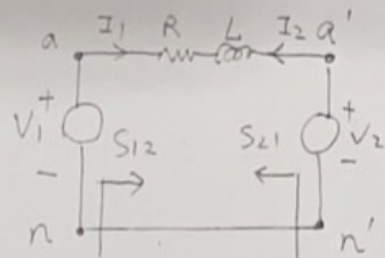


圖 2.14 單相電路

可推導 (2.26) $S_{12} = V_1 \cdot I_1^*$, 因為 $I_1 = \frac{V_1 - V_2}{Z}$

$$S_{12} = V_1 \cdot \left(\frac{V_1 - V_2}{Z} \right)^* = \frac{V_1 \cdot V_1^* - V_1 \cdot V_2^*}{Z^*}$$

$$= \frac{|V_1|^2 - |V_1| \cdot |V_2| e^{j\theta_{12}}}{|Z| \cdot e^{-j\angle Z}} = \frac{|V_1|^2}{|Z|} \cdot e^{j\angle Z} - \frac{|V_1| |V_2|}{|Z|} e^{j\angle Z} \cdot e^{-j\theta_{12}}$$

可推導 (2.27) $S_{21} = V_2 \cdot I_2^*$, 因為 $I_2 = \frac{V_2 - V_1}{Z}$

$$S_{21} = V_2 \cdot \left(\frac{V_2 - V_1}{Z} \right)^* = \frac{|V_2|^2}{|Z|} \cdot e^{j\angle Z} - \frac{|V_2| |V_1|}{|Z|} \cdot e^{j\angle Z} \cdot e^{-j\theta_{12}}$$

所以 (2.28) $-S_{21} = -\frac{|V_2|^2}{|Z|} \cdot e^{j\angle Z} + \frac{|V_2| |V_1|}{|Z|} \cdot e^{j\angle Z} \cdot e^{-j\theta_{12}}$

(2.29) $S_{12} = C_1 - B e^{j\theta_{12}}$, (2.30) $-S_{21} = C_2 + B e^{-j\theta_{12}}$

送端圓圓心 $C_1 = \frac{|V_1|^2}{|Z|} e^{j\angle Z}$, 受端圓圓心 $C_2 = -\frac{|V_2|^2}{|Z|} e^{j\angle Z}$, 半徑 $B = \frac{|V_1| |V_2|}{|Z|} e^{j\angle Z}$

簡化, 假設 $R=0$, $Z = j\omega L = jX \Rightarrow |Z| = X$, $\angle Z = 90^\circ$, 代入 (2.26) 和 (2.27)

(2.26) $S_{12} = \frac{|V_1|^2}{|Z|} \cdot (\cos 90^\circ + j \sin 90^\circ) - \frac{|V_1| |V_2|}{|Z|} \cdot (\cos 90^\circ + j \sin 90^\circ) \cdot (\cos \theta_{12} + j \sin \theta_{12})$

$$= j \frac{|V_1|^2}{X} - j \frac{|V_1| |V_2|}{X} \cos \theta_{12} + \frac{|V_1| |V_2|}{X} \sin \theta_{12} = P_{12} + j Q_{12}$$

所以實功 $P_{12} = \frac{|V_1| |V_2|}{X} \sin \theta_{12}$ (2.31), $Q_{12} = \frac{|V_1|^2}{X} - \frac{|V_1| |V_2|}{X} \cos \theta_{12}$ (2.32)

(2.27) $S_{21} = \frac{|V_2|^2}{|Z|} \cdot (\cos 90^\circ + j \sin 90^\circ) - \frac{|V_2| |V_1|}{|Z|} \cdot (\cos 90^\circ + j \sin 90^\circ) \cdot (\cos(-\theta_{12}) + j \sin(-\theta_{12}))$


$$= j \frac{|V_2|^2}{X} - j \frac{|V_1| |V_2|}{X} \cos \theta_{12} - \frac{|V_1| |V_2|}{X} \sin \theta_{12} = P_{21} + j Q_{21}$$

所以實功 $P_{21} = -\frac{|V_1| |V_2|}{X} \sin \theta_{12} = -P_{12}$


$Q_{21} = \frac{|V_2|^2}{X} - \frac{|V_2| |V_1|}{X} \cos \theta_{12}$ (2.33)

2022/04/19 電力工程導論 姓名_____ 學號_____

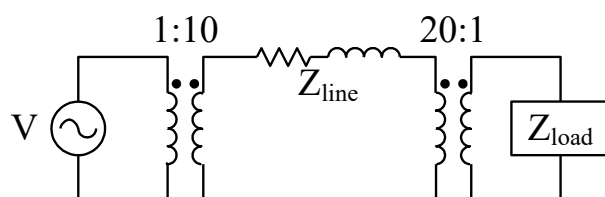
1. (10) Compare DC power system with AC power system.
2. (10) Compare AC single phase voltage with three phase voltage.
3. (10) A generator will be paralleled with a running AC power system. Which conditions are required for paralleling?
4. (10) Plotting the generator phasor diagrams under (a) lagging power factor; (b) unity power factor; (c) leading power factor.
5. (20) A simple power system is shown in figure. This system contains a 480V(0°)/60Hz generator connected to an ideal 1:10 step-up transformer, a transmission line, an ideal 20:1 step-down transformer, and a load. The impedance of the transmission line is $Z_{\text{line}} = 20 + j60\Omega$, and $Z_{\text{load}} = 8.66 + j5\Omega$. The base values for this system are chosen to be 480V and 10kVA at the generator.
 - (a) Find the base voltage, current, impedance, and apparent power at every point in the power system.
 - (b) Convert this system to its per-unit equivalent circuit.
 - (c) Find the power supplied to the load in this system.
 - (d) Find the power lost in the transmission line



6. (20) $S_{G1}: V_1 = 1 \angle 0^\circ$, $S_{D1} = 1$, $jQ_{G2}: V_2 = ?$, $S_{D2} = 1$, $Z = j0.5$, (a) Find Q_{G2} for $|V_2| = 1$ (b) and $\angle V_2$? (c) If $Q_{G2} = 0$, could be supplied load S_{D2} ? (d) and $\angle V_2$?

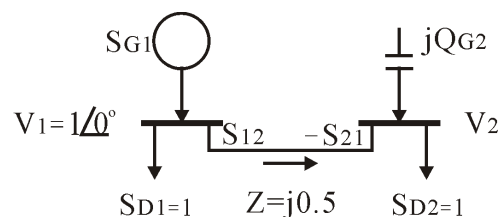

7. (20) Find (a) S_{12} and S_{21} ; (b) P_{12} and $-P_{21}$; (c) Q_{12} and Q_{21} .
 ($Z = R + j\omega L$, $V_1 = |V_1|e^{j\theta_1}$, $V_2 = |V_2|e^{j\theta_2}$, $Z = |Z|e^{j\angle Z}$, $\theta_{12} = \theta_1 - \theta_2$)

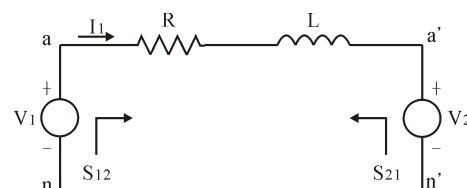


1. (10) Compare DC power system with AC power system.

直流電力系統

①: 電感短路, 電容開路,
∴ 沒有虛功.

② 傳統的無源升壓降壓轉換: 近代靠電力電子


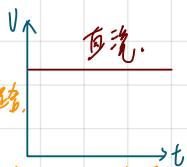


交流電力系統


① 介: 單相及三相

② 電感、電容不能忽略,
∴ 產生虛功.

③ 利用變壓器升壓 ∴ 減少傳輸線損失再降壓提供負載使用.

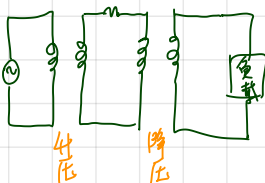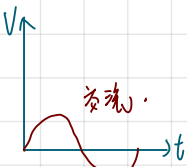


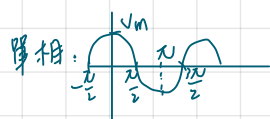2. (10) Compare AC single phase voltage with three phase voltage.



$$v(t) = V_m \cdot \sin \omega t$$

缺點: Power 脈動.
電力是抖動的

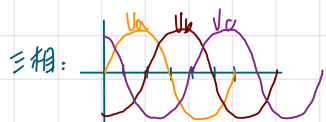

優點: Power 是常數 = $3 \cdot V_{\text{相}} \cdot I_{\text{相}} \cos \theta = \sqrt{3} V_{\text{line-to-line}} \cdot I_{\text{line-to-line}} \cos \theta$
(線對線)

$$v_a(t) = V_m \cdot \sin \omega t$$

$$v_b(t) = V_m \cdot \sin(\omega t - 120^\circ) = V_m \sin(\omega t - \frac{2}{3}\pi)$$

$$v_c(t) = V_m \cdot \sin(\omega t - 240^\circ)$$


3. (10) A generator will be paralleled with a running AC power system. Which conditions are required for paralleling?

併網條件: ① 頻率 (f 頻率, $\omega = 2\pi f$ 角速度) 一樣,
② 角度一樣
③ 相序一樣
④ V_m (振幅) 一樣,

4. (10) Plotting the generator phasor diagrams under (a) lagging power factor; (b) unity power factor; (c) leading power factor.


相量圖在同步座標.

(a) 落後功因, (b) 單位功因, (c) 領先功因.

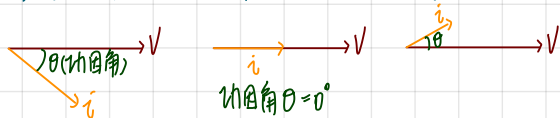

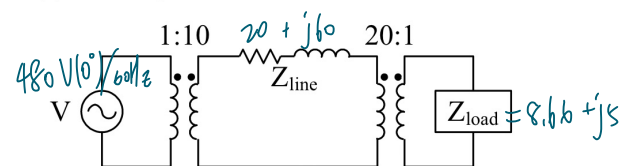5.(20) A simple power system is shown in figure. This system contains a 480V(0°)/60Hz generator connected to an ideal 1:10 step-up transformer, a transmission line, an ideal 20:1 step-down transformer, and a load. The impedance of the transmission line is $Z_{line} = 20 + j60 \Omega$, and $Z_{load} = 8.66 + j5 \Omega$. The base values for this system are chosen to be 480V and 10kVA at the generator.

- Find the base voltage, current, impedance, and apparent power at every point in the power system.
- Convert this system to its per-unit equivalent circuit.
- Find the power supplied to the load in this system.
- Find the power lost in the transmission line



(a) I. In the generator region:

$$V_{base1} = 480 \text{ V}; S_{base} = 10 \text{ kVA} = 10000 \text{ VA}.$$

$$I_{base1} = \frac{S_{base}}{V_{base1}} = \frac{10000 \text{ VA}}{480 \text{ V}} = 20.83 \text{ A}.$$

$$Z_{base1} = \frac{V_{base1}}{I_{base1}} = \frac{480 \text{ V}}{20.83 \text{ A}} = 23.04 \Omega.$$

II. In the transmission line region:

$$V_{base2} = 10 \cdot V_{base1} = 10 \times 480 = 4800 \text{ V}; S_{base} = 10000 \text{ VA}.$$

$$I_{base2} = \frac{S_{base}}{V_{base2}} = \frac{10000 \text{ VA}}{4800 \text{ V}} = 2.083 \text{ A}.$$

$$Z_{base2} = \frac{V_{base2}}{I_{base2}} = \frac{4800 \text{ V}}{2.083 \text{ A}} = 2304 \Omega.$$

III. In the load region:

$$V_{base3} = \frac{1}{20} V_{base2} = \frac{1}{20} \times 4800 = 240 \text{ V}; S_{base} = 10000 \text{ VA}.$$

$$I_{base3} = \frac{S_{base}}{V_{base3}} = \frac{10000 \text{ VA}}{240 \text{ V}} = 41.67 \text{ A}.$$

$$Z_{base3} = \frac{V_{base3}}{I_{base3}} = \frac{240 \text{ V}}{41.67 \text{ A}} = 5.76 \Omega.$$

(b) I. In the generator region:

$$V_{G,pu} = \frac{V_G}{V_{base1}} = \frac{480 \angle 0^\circ \text{ V}}{480 \text{ V}} = 1.0 \angle 0^\circ \text{ pu}.$$

II. In the transmission line region:

$$Z_{line,pu} = \frac{Z_{line}}{Z_{base2}} = \frac{20 + j60 \Omega}{2304 \Omega} = 0.0087 + j0.026 \text{ pu}.$$

III. In the load region:

$$Z_{load,pu} = \frac{Z_{load}}{Z_{base3}} = \frac{8.66 + j5 \Omega}{5.76 \Omega} = 1.503 + j0.868 \text{ pu}.$$

$$(c) I_{pu} = \frac{V_{pu}}{Z_{tot,pu}} = \frac{1 \angle 0^\circ}{0.0087 + j0.026 + 1.503 + j0.868 \text{ pu}} = 0.4901 - j0.2898 \text{ pu} = 0.569 \angle -30.6^\circ \text{ pu}.$$

$$P_{load,pu} = I_{pu}^2 \cdot P_{load,pu} = (0.569)^2 \cdot 1.503 = 0.489.$$

$$P_{load} = P_{load,pu} \cdot S_{base} = 0.489 \times 10000 \text{ VA} = 4890 \text{ W}.$$


$$(d) P_{line,pu} = I_{pu}^2 R_{line,pu} = (0.569)^2 (0.0087) = 0.00282$$

$$P_{line} = P_{line,pu} S_{base} = 0.00282 \times 10000 \text{ VA} = 28.2 \text{ W}$$

shift + 2, diff 3.




6.(20) $S_{G1}: V_1=1 \angle 0^\circ, S_{D1}=1, jQ_{G2}: V_2=? \rightarrow S_{D2}=1, Z=j0.5$, (a) Find Q_{G2} for $|V_2|=1$ (b) and $\angle V_2$? (c) If $Q_{G2}=0$, could be supplied load S_{D2} ? (d) and $\angle V_2$?

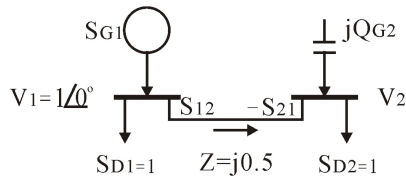

$$S = P + jQ$$

$$\begin{cases} P_{12} = -P_{21} = \frac{|V_1||V_2|}{X} \sin \theta_{12} \\ Q_{12} = \frac{|V_1|^2}{X} - \frac{|V_1||V_2|}{X} \cos \theta_{12} \\ Q_{21} = \frac{|V_2|^2}{X} - \frac{|V_1||V_2|}{X} \cos \theta_{12} \end{cases}$$

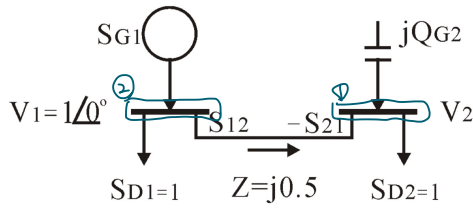

$$\textcircled{1} jQ_{G2} - S_{21} = 1 \Rightarrow \frac{P_{21}}{S_{P_{12}}=1}; Q_{21} = Q_{G2}$$

$$\textcircled{2} S_{G1} = 1 + S_{12}$$

$$\Rightarrow S_{12} = -1$$

$$\textcircled{1} \textcircled{2} Q_{G2} = 0, \text{ find } S_{D2} \text{ \& } \angle V_2$$

Method I.

$$Q_{G2} = 0 \Rightarrow Q_{21} = \frac{|V_2|^2}{X} - \frac{|V_1||V_2|}{X} \cos \theta_{12} = 0$$

$$\Rightarrow |V_2| = |V_1| \cos \theta_{12}$$

$$\Rightarrow |V_2| = \cos \theta_{12} \Rightarrow \theta_{12} = 0$$


$$P_{12} = \frac{|V_1||V_2|}{X} \sin \theta_{12} = 1$$

$$\Rightarrow |V_2| \sin \theta_{12} = \frac{1}{2} \textcircled{2}$$

Method II.

$$\textcircled{1} \textcircled{2}: C_2 = -\frac{|V_2|^2}{|Z|} e^{j\angle Z} = -2|V_2|^2 j$$

$$\text{Magnitude: } |B| = \frac{|V_1||V_2|}{|Z|} = 2|V_2|$$

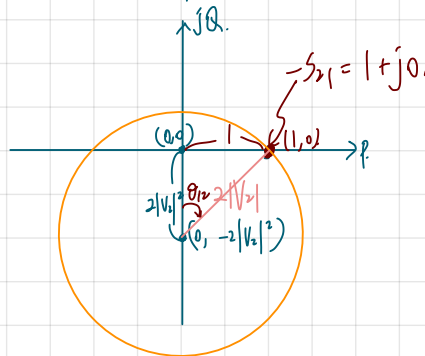

$$1^2 + (2|V_2|^2)^2 = 4|V_2|^2$$

$$4(|V_2|^2)^2 - 4|V_2|^2 + 1 = 0$$

$$\Rightarrow |V_2|^2 = \frac{1}{2} \Rightarrow |V_2| = \frac{1}{\sqrt{2}}$$

$$\Rightarrow \theta_{12} = 45^\circ \Rightarrow \angle V_2 = -45^\circ$$

(a) (b) $|V_2|=1$. Find $Q_{G2}, \angle V_2$

$$P_{12} = \frac{|V_1||V_2|}{X} \sin \theta_{12} = 1$$

$$\Rightarrow \frac{1 \times 1}{0.5} \sin \theta_{12} = 1$$

$$\Rightarrow \sin \theta_{12} = \frac{1}{2} \Rightarrow \theta_{12} = 30^\circ$$

$$\Rightarrow \theta_{12} = \theta_1 - \theta_2 = 30^\circ$$

$$\theta_2 = \theta_1 - 30^\circ = -30^\circ \therefore \angle V_2 = -30^\circ \#$$


$$Q_{G2} = Q_{21} = \frac{|V_2|^2}{X} - \frac{|V_1||V_2|}{X} \cos \theta_{12}$$

$$= \frac{1}{0.5} - \frac{1}{0.5} \cos 30^\circ$$

$$= 2 - 2 \cos 30^\circ = 0.2679 \#$$

7. (20) Find (a) S_{12} and S_{21} ; (b) P_{12} and $-P_{21}$; (c) Q_{12} and Q_{21} .

($Z=R+j\omega L$, $V_1=|V_1|e^{j\theta_1}$, $V_2=|V_2|e^{j\theta_2}$, $Z=|Z|e^{j\angle Z}$, $\theta_{12}=\theta_1-\theta_2$)

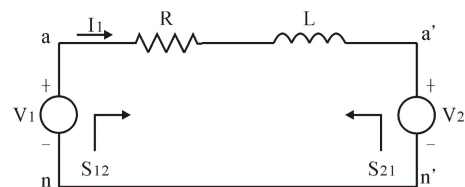

功率圓(短程) Complex power Circle

短程輸電線，用串聯的RL電路來表示電線 $Z=R+j\omega L$

$$(2.25) V_1=|V_1|e^{j\theta_1}, V_2=|V_2|e^{j\theta_2}, Z=|Z|e^{j\angle Z}, \theta_{12}=\theta_1-\theta_2$$

$$(2.26) S_{12}=V_1 I_1^*=V_1[(V_1-V_2)/Z]^*=|V_1|^2/(Z)^*-V_1 V_2^*/(Z)^* \\ =|V_1|^2 e^{j\angle Z}/|Z|-|V_1||V_2| e^{j\angle Z}e^{j\theta_{12}}/|Z|$$

$$(2.27) S_{21}=|V_2|^2 e^{j\angle Z}/|Z|-|V_1||V_2| e^{j\angle Z}e^{-j\theta_{12}}/|Z|$$

$$(2.28) -S_{21}=-|V_2|^2 e^{j\angle Z}/|Z|+|V_1||V_2| e^{j\angle Z}e^{-j\theta_{12}}/|Z|$$

$$(2.29) S_{12}=C_1-B e^{j\theta_{12}}, \quad \text{兩圓半徑均為 } |B|$$

$$(2.30) -S_{21}=C_2+B e^{-j\theta_{12}},$$

$$C_1=|V_1|^2 e^{j\angle Z}/|Z|, C_2=-|V_2|^2 e^{j\angle Z}/|Z|,$$


$$B=|V_1||V_2| e^{j\angle Z}/|Z|,$$

Assume $R=0$, $Z=jX \Rightarrow \angle Z=90^\circ$, $e^{j\angle Z}=j$

$$\text{So } (2.31) P_{12}=-P_{21}=(|V_1||V_2|/X)\sin\theta_{12}$$

$$(2.32) Q_{12}=|V_1|^2/X - (|V_1||V_2|/X)\cos\theta_{12}$$


$$(2.33) Q_{21}=|V_2|^2/X - (|V_1||V_2|/X)\cos\theta_{12}$$

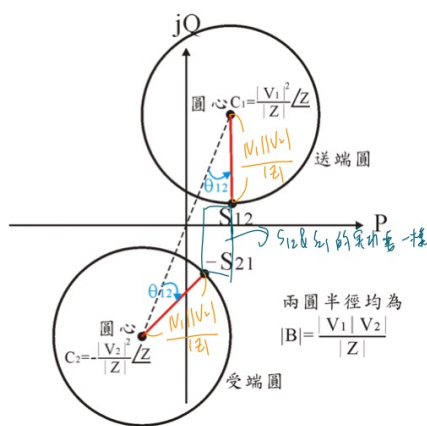

s/b (五) 考試, (二四 B2b)
 * 可帶筆記, 計算機, 平板 (可查資料...), 書

1. (10) Compare DC power system with AC power system.


直流電力系統

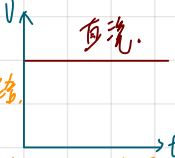

① 電感短路, 電容開路,
 ∴ 沒有虛功.


② 傳統的無條件降壓轉換; 近代靠電力電子

交流電力系統

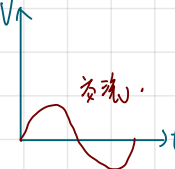

① 分: 單相 & 三相
 ② 電感、電容不能忽略。
 ∴ 產生虛功.

③ 利用變壓器升壓 ∴ 減少傳輸線損失再降壓提供負載使用.

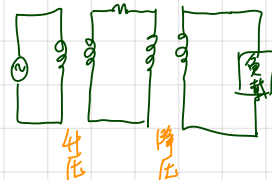

2. (10) Compare AC single phase voltage with three phase voltage.


單相:



缺點: Power 脈動.
 電力是抖動的

$v(t) = V_m \cdot \sin \omega t$

三相:

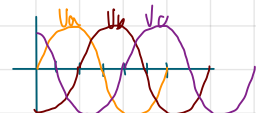

優點: Power 是常數 $= 3 \cdot V_{相} \cdot I_{相} \cos \theta = \sqrt{3} V_{line-to-line} \cdot I_{line-to-line} \cos \theta$
 (線對線)



$v_a(t) = V_m \cdot \sin \omega t$
 $v_b(t) = V_m \cdot \sin(\omega t - 120^\circ) = V_m \sin(\omega t - \frac{2}{3}\pi)$
 $v_c(t) = V_m \cdot \sin(\omega t - 240^\circ)$

3. (10) A generator will be paralleled with a running AC power system. Which conditions are required for paralleling?

併網條件: ① 頻率 (f (頻率) $\omega = 2\pi f$ (角速度)) 一樣.
 ② 角度一樣
 ③ 相序一樣
 ④ V_m (振幅) 一樣.


4. (10) Plotting the generator phasor diagrams under (a) lagging power factor; (b) unity power factor; (c) leading power factor.


相量圖在同步座標.
 (a) 落後功因, (b) 單位功因, (c) 領先功因.

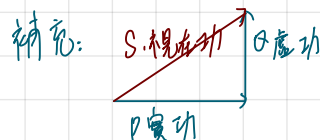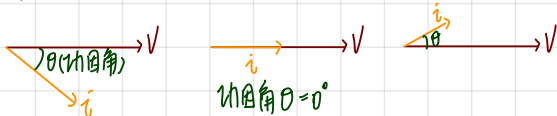

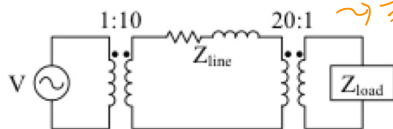5. (20) A simple power system is shown in figure. This system contains a 480V (0°)/60Hz generator connected to an ideal 1:10 step-up transformer, a transmission line, an ideal 20:1 step-down transformer, and a load. The impedance of the transmission line is $Z_{line} = 20 + j60 \Omega$, and $Z_{load} = 8.66 + j5 \Omega$. The base values for this system are chosen to be 480V and 10kVA at the generator.

- Find the base voltage, current, impedance, and apparent power at every point in the power system.
- Convert this system to its per-unit equivalent circuit.
- Find the power supplied to the load in this system.
- Find the power lost in the transmission line



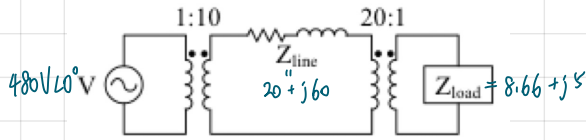

Q: 标准电压 480V, 10kVA.

(a) 表准 (V, i, 阻抗, 视在功)

(b) 简化成标准图

(c) 负载的真实功率.

(d) 传输线损.

课本有答案,

也在讲义 CH2. EX2-3, 有ANS.

A: 发电机 $V_b = 480$, $S_b = 10 \text{ kVA} \Rightarrow \frac{480}{480} = 1 \angle 0^\circ$ (标准)

传输线 $V_b = 4800$, $S_b = 10 \text{ kVA}$.

$$\Rightarrow S_b = V_b \cdot I_b \Rightarrow I_b = \frac{10 \text{ kVA}}{4800} \Rightarrow Z_b = \frac{V_b}{I_b} = \frac{4800}{\left(\frac{10 \text{ kVA}}{4800}\right)}$$

$$\text{阻抗} \frac{20 + j60}{Z_b}$$

$$\text{负载 } V_b = 240, S_b = 10 \text{ kVA} \Rightarrow I_b = \frac{10 \text{ kVA}}{240} \Rightarrow Z_b = \frac{V_b}{I_b} = \frac{240}{\left(\frac{10 \text{ kVA}}{240}\right)}$$

$$\text{阻抗} \frac{8.66 + j5}{Z_b}$$

bus2: 流进虚功 = 流出虚功.

流进实功 = 流出实功.

$$P_{12} = S_{12} = 1$$



$$I = \frac{V_1 |V_2|}{X} \sin \theta_{12}; Z = j0.5 = jX = j\omega L$$

$$\text{已知 } \begin{cases} |V_1| = 1 \\ |V_2| = 1 \end{cases} \Rightarrow X = 0.5 \Rightarrow \sin \theta_{12} = 0.5, \theta_{12} = 30^\circ \Rightarrow V_2 = 1 \angle -30^\circ$$

6.(20) $S_{G1}: V_1 = 1 \angle 0^\circ$, $S_{D1} = 1$, $jQ_{G2}: V_2 = ?$, $S_{D2} = 1$, $Z = j0.5$, (a) Find Q_{G2} for $|V_2| = 1$

(b) and $\angle V_2$? (c) If $Q_{G2} = 0$, could be supplied load S_{D2} ? (d) and $\angle V_2$?

CH2 EX2.14.

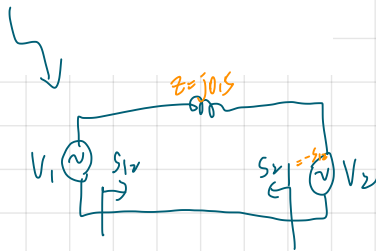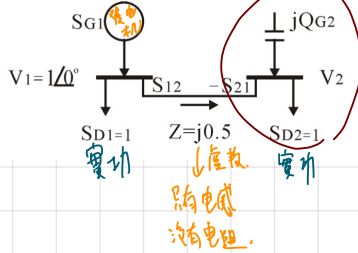

① θ_{12} , $V_2 = ?$

(a) $|V_2| = 1$

(b) $\angle V_2 = ?$

(c) $Q_{G2} = 0$.



(d) $\angle V_2 = ?$

7. (20) Find (a) S_{12} and S_{21} ; (b) P_{12} and $-P_{21}$; (c) Q_{12} and Q_{21} .

($Z=R+j\omega L$, $V_1=|V_1|e^{j\theta_1}$, $V_2=|V_2|e^{j\theta_2}$, $Z=|Z|e^{j\angle Z}$, $\theta_{12}=\theta_1-\theta_2$)

CH2

Ex 2.12

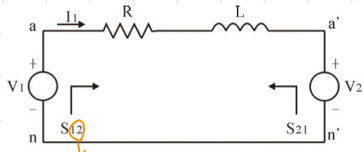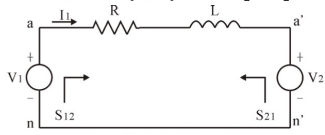

從1到2的功率在功。

$$S_{12} = V_1 \cdot I_1^* \quad \text{⊗} \rightarrow \text{共轭} \quad \rightarrow \text{see CH2 式(2.5)}$$

$$Z = R + j\omega L \rightarrow \begin{matrix} j\omega L \\ \uparrow \\ R \end{matrix} \quad \begin{matrix} \theta \\ \nearrow \end{matrix}$$

$$|Z| = \sqrt{R^2 + (\omega L)^2}, \quad \tan \theta = \frac{\omega L}{R}$$

$$\rightarrow Z = |Z|e^{j\theta}$$

(a) $S_{12} = V_1 I_1^*$

$$S_{21} = V_2 (-I_1)^*$$

$$I_1 = \frac{V_1 - V_2}{Z}$$

$$S_{12} = V_1 \cdot \left(\frac{V_1 - V_2}{Z} \right)^*$$

$$= V_1 \left(\frac{V_1^* - V_2^*}{Z^*} \right) \quad \rightarrow S_{12} \text{ 的 answer 爲 CH2 的式 (2.16)}$$

$$S_{21} = V_2 \left(\frac{V_2 - V_1}{Z} \right)^*$$

$$= V_2 \left(\frac{V_2^* - V_1^*}{Z^*} \right) \quad \text{式 (2.17)}$$

Assume $R=0$: P_{12} & $-P_{21}$ 相等: 式 (2.31)